

UNIVERSITY OF TORONTO
FACULTY OF APPLIED SCIENCE AND ENGINEERING

ECE 110H1 S -- ELECTRICAL FUNDAMENTALS
FINAL EXAMINATION, APRIL 23, 2018, 6:30 pm

First Year -- Computer, Electrical, Industrial, Mechanical, Materials,
and Track One Engineering Programs.

Examiners – S. Aitchison, B. Bardakjian, M. Mojahedi, B. Wang and P. Yoo

($e = 1.6 \times 10^{-19}$ C, $\epsilon_0 = 8.85 \times 10^{-12}$ F/m, $\mu_0 = 4\pi \times 10^{-7}$ H/m, $g = 9.81$ N/kg)

NAME :

(PLEASE PRINT)

Family (Last) Name

Given (First) Name

STUDENT NUMBER :

EXAMINATION TYPE : D (Students may use a single double sided 8.5" x 11" aid sheet)

CALCULATORS : Casio FX-991 (EX, EX Plus, or MS), Sharp EL-520 (X or W)

DURATION : 2.5 hours

INSTRUCTIONS :


- Answer all five questions. Put the answers in the boxes provided.
- All work is to be done on these pages. Show steps, compute numerical results when requested and state units. Write down any assumption made.
- You may use the back of each page.
- Last blank page may be removed for rough work.

Question	Mark
1	
2	
3	
4	
5	
Total	

Q1 [10 marks] Multiple Choice Questions Section 1

Circle the correct answer for each part.

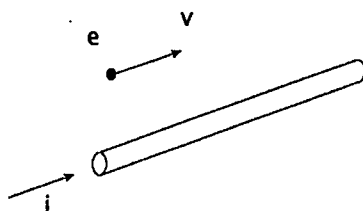
(a) [2 marks] A long wire carries a current, i , as shown in the figure below. An electron is launched parallel to the wire with a velocity, v as shown. Which of the following statements is true?



- The electron moves in a straight line parallel to the wire.
- The electron moves in an arc towards the wire.
- The electron moves in an arc away from the wire.
- The electron slows down and continues to move parallel to the wire
- The electron speeds up and continues to move parallel to the wire

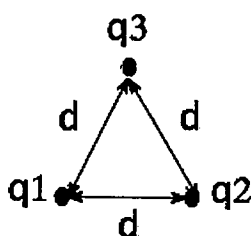(b) [2 marks] Three charges are placed on the corners of an equilateral triangle, as shown below. Which expression describes the electric potential at point P, at the center of the triangle?


(Hint: $\cos 30^\circ = \frac{\sqrt{3}}{2}$)



- $V = 0$
- $V = \frac{\sqrt{3}}{4\pi\epsilon_0 d} (q_1 + q_2 + q_3)$
- $V = \frac{\sqrt{3}}{4\pi\epsilon_0 d^2} (q_1 + q_2 + q_3)$
- $V = \frac{3}{4\pi\epsilon_0 d^2} (q_1 + q_2 + q_3)$
- $V = \frac{\sqrt{3}}{4\pi\epsilon_0 d} (q_1 q_2 + q_1 q_3 + q_2 q_3)$


Q1 continued

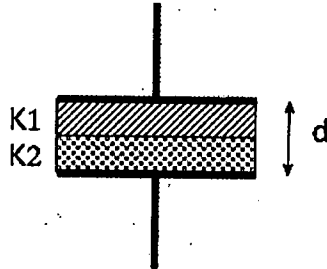(c) [2 marks] The parallel plate capacitor shown in the figure below consists of two plates of area A , separated by a distance d . The capacitor contains two slabs of dielectric material, with equal thickness, with dielectric constants K_1 and K_2 . Which of the following expressions for the capacitance is correct?



- a. $C = \frac{\epsilon_0 A}{d}$
- b. $C = \frac{\epsilon_0 A}{d} \left(\frac{K_1 + K_2}{K_1 K_2} \right)$
- c. $C = \frac{\epsilon_0 A}{d} (K_1 K_2)$
- d. $C = \frac{2\epsilon_0 A}{d} \left(\frac{K_1 K_2}{K_1 + K_2} \right)$
- e. $C = \frac{\epsilon_0 A}{d} (K_1 + K_2)$

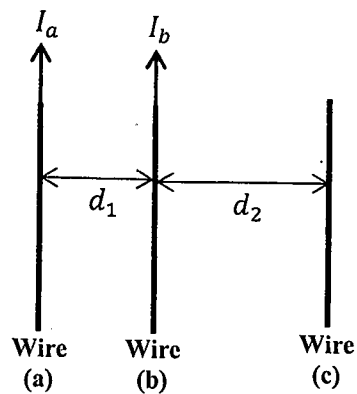(d) [2 marks] Figure shows three very long and thin wires carrying currents: I_a , I_b , and I_c (I_c is not shown on the figure). If $d_2 = 2d_1$ and wire (b) experiences *no force due to the currents*, what should be the direction of I_c and the ratio I_c/I_a ?



- a. I_c flows from the **bottom to top** with $I_c/I_a = 0.5$
- b. I_c flows from the **top to bottom** with $I_c/I_a = 0.5$
- c. I_c flows from the **bottom to top** with $I_c/I_a = 2$
- d. I_c flows from the **top to bottom** with $I_c/I_a = 2$

Q1 continued

(e) [2 marks] A closed sphere, radius R , is placed close to a long wire, current carrying a current, i . Which expression describes the magnetic flux through the sphere.

- a. $\mu_0 i$
- b. $\frac{\mu_0 i}{(4\pi R^2)}$
- c. $4\pi R^2 \mu_0 i$
- d. 0
- e. $\frac{4}{3}\pi R^2 \mu_0 i$

Q2 [10 marks] Multiple Choice Questions Section 2

Circle the correct answer for each part.

(a) [2 marks] A closed loop of wire, with total resistance, R , moves with constant velocity v , parallel to an infinity long wire which carries a current i , as shown below. Which of the following is true?



- The current induced in the wire is in the clockwise direction.
- There is no current induced in the wire.
- The current in the wire oscillates between clockwise and anti-clockwise
- The current induced in the wire is in the anticlockwise direction.

(b) [2 marks] Voltage across an inductor, $L = 2 [H]$, is given by

For $-\infty < t < 0 [s]$, $v(t) = 0 [V]$

For $0 < t < 10 [s]$, $v(t) = 6 t^2 [V]$

For $10 < t < \infty [s]$, $v(t) = 0 [V]$

Circle the correct value of the current at $t = 4 [s]$

- 18 [A]
- 128 [A]
- 64 [A]
- 56 [A]

(c) [2 marks] Consider the Kirchhoff Voltage Law (KVL) and Kirchhoff Current Law (KCL).

Circle the correct statement below.

- KVL is a statement of conservation of charges and KCL is a statement of conservation of energy.
- KVL is a statement of conservation of energy and KCL is a statement of conservation of charges.
- KVL is a statement of conservation of volume and KCL is a statement of conservation of current.
- None of the above.

Q2 continued

(d) [2 marks] Circle the correct statement.


- a. For a capacitor, both voltage and current must be continuous functions of time.
- b. For a capacitor, voltage must be a continuous function of time; however, current can be a discontinuous function of time.
- c. For a capacitor, current must be a continuous function of time; however, voltage can be a discontinuous function of time.
- d. None of the above statements is correct.

(e) [2 marks] Considering the voltage across and current through a capacitor in an AC circuit, circle the correct statement.

- a. Current leads the voltage by 90 degree.
- b. Voltage leads the current by 90 degree.
- c. Current and voltage are in phase (neither leads or lags the other).
- d. None of the above.

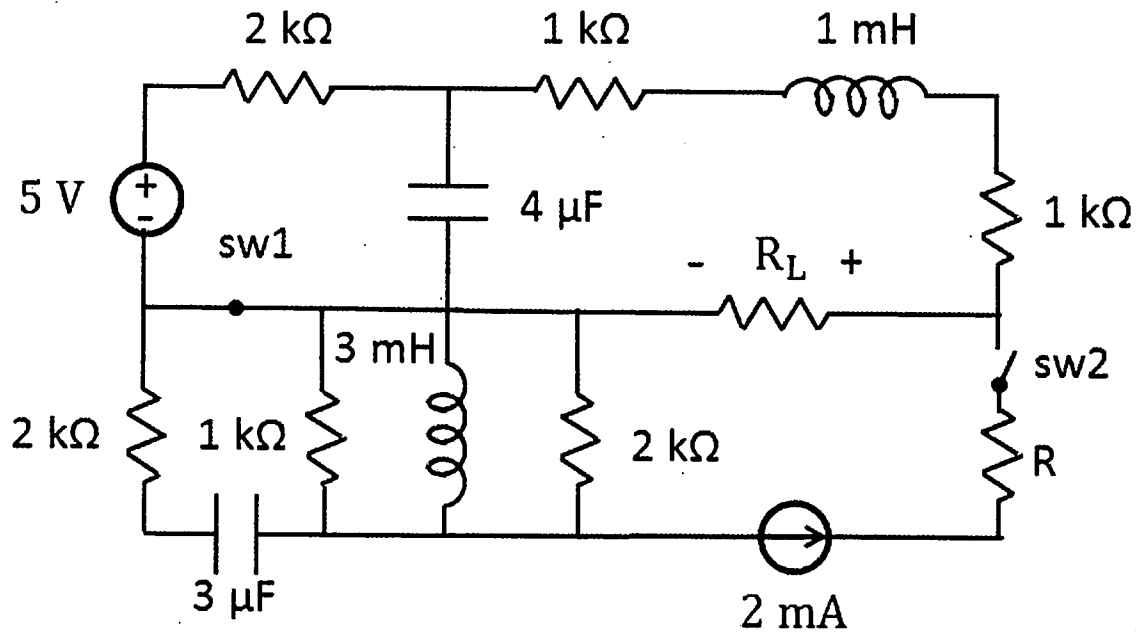Q3 [10 marks]


Consider the following circuit under DC conditions, where independent voltage (5 volts) and current (2 mA) sources are used to deliver electrical energy to multiple circuit elements. There are 2 switches (sw1 & sw2) that can be independently controlled to be in either the open or closed position.



- (a) [4 marks] When sw1 is closed and sw2 is open, as shown above. Determine R_L such that maximum power is transferred to the load resistor. Assume $R = 10\text{ k}\Omega$.

$R_L =$


Q3 continued.

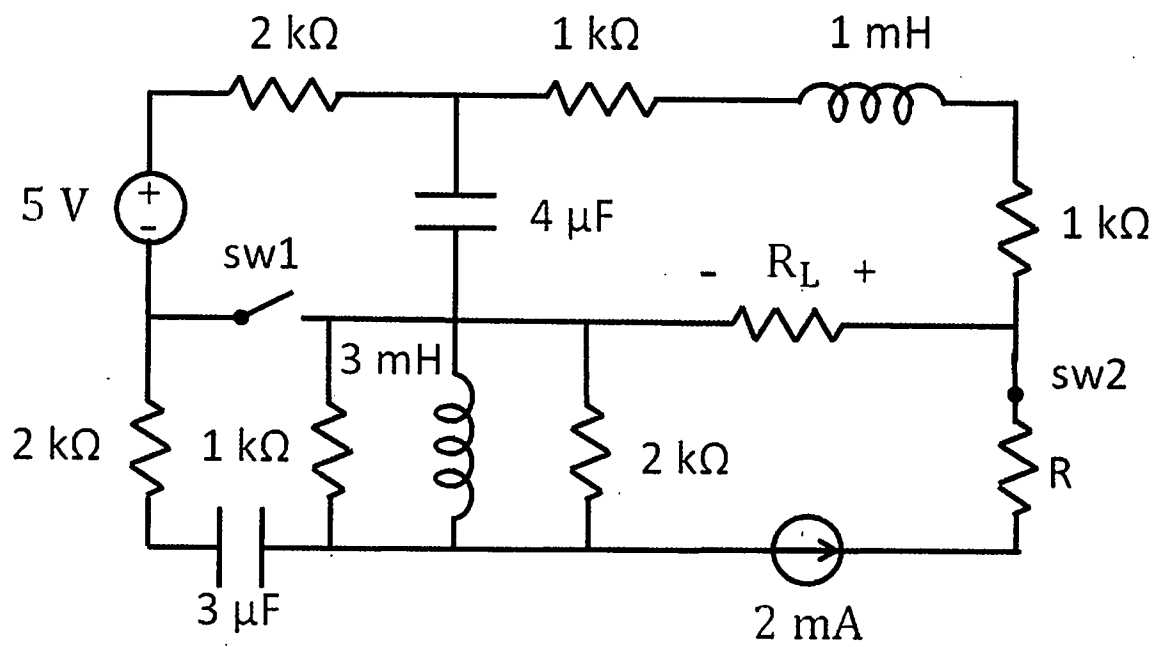

(b) [2 marks] In the case where sw1 is open and sw2 is closed, shown above, determine the value of a replacement resistor, R such that the power dissipated by this resistor is equal to the power dissipated by R_L in part (a). (Use the same value of R_L)

$R =$

Q3 continued.

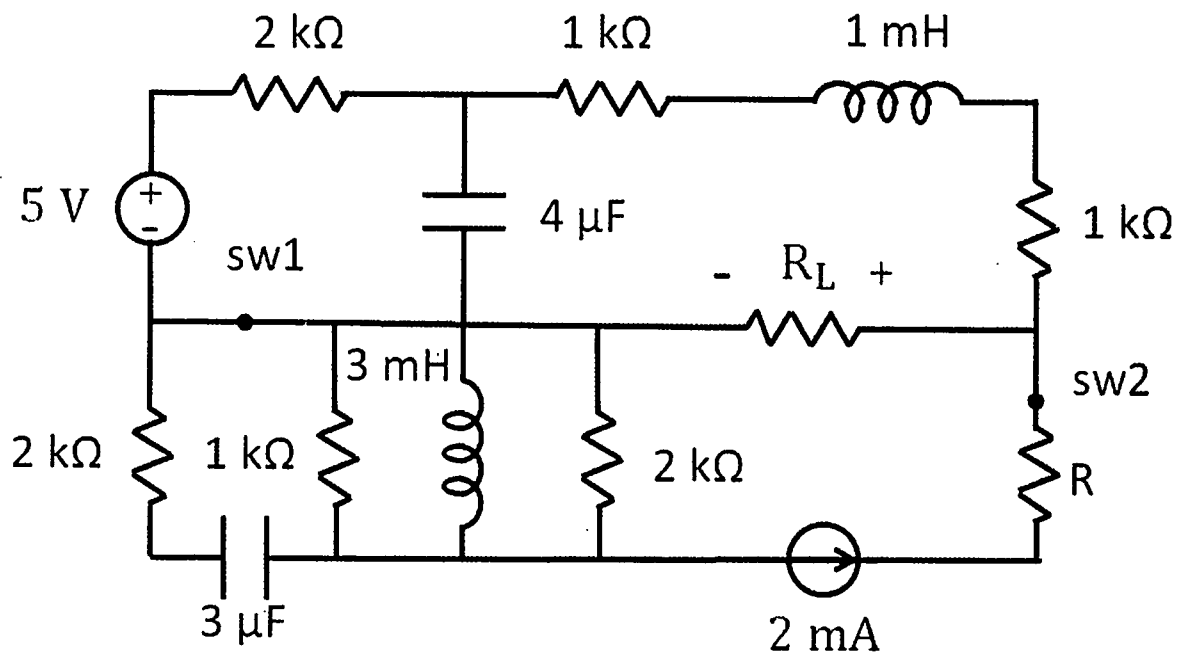

(c) [4 marks] If both sw1 & sw2 are closed, determine the Norton equivalent circuit that would allow maximum power transfer to a given R_L . Assume $R = 2\text{ k}\Omega$.

Norton Equivalent Circuit:

+


•

•

-

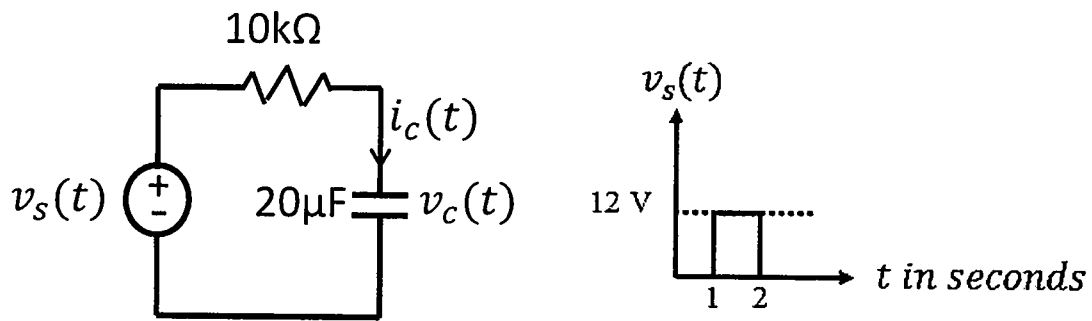Q4 [10 marks]


A pulse voltage source $v_s(t)$ is applied to the series RC circuit shown below.



(a) [6 marks] Determine the capacitor voltage $v_c(t)$.

$v_c(t) =$

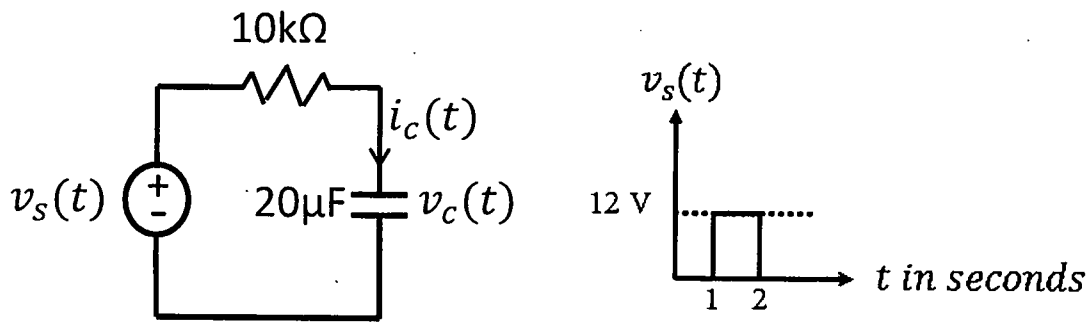Q4 continued. (Circuit diagram and pulse diagram have been duplicated for your convenience)



(b) [2 marks] Determine the capacitor current $i_c(t)$.

$$i_c(t) =$$


(c) [2 marks] Determine the energy stored in the capacitor at $t_1 = 1 + \tau$ and $t_2 = 2 + \tau$, where t_1 , & t_2 are time in seconds, and τ is the time constant of the circuit.

$$\text{Energy}_{t_1} =$$

$$\text{Energy}_{t_2} =$$

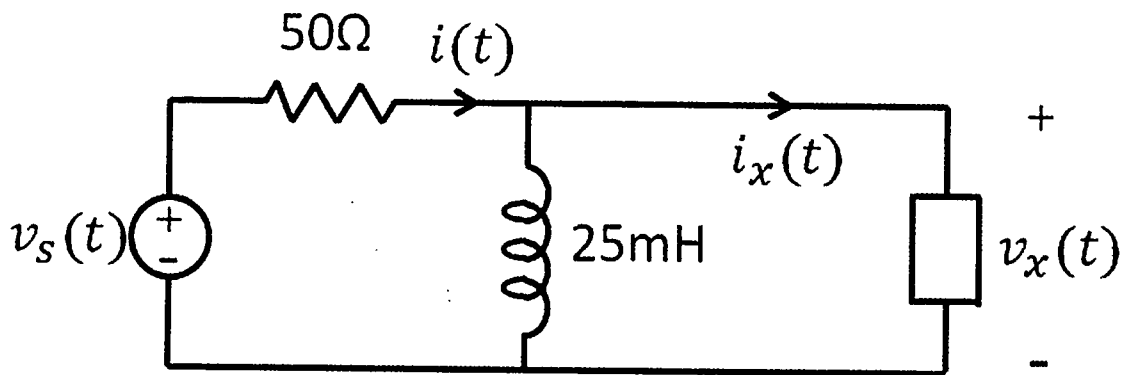Q5 [10 marks]

The circuit shown below is operating in the sinusoidal steady state with $v_s(t) = 50 \cos(2000t - 20^\circ)$ V and $i(t) = 0.5 \cos(2000t)$ A.




(a) [1 mark] Draw the circuit in the frequency domain, indicating all phasors and impedances.

(b) [4 marks] Find the phasor voltage, V_x and the phasor current, I_x .

$V_x =$

$I_x =$

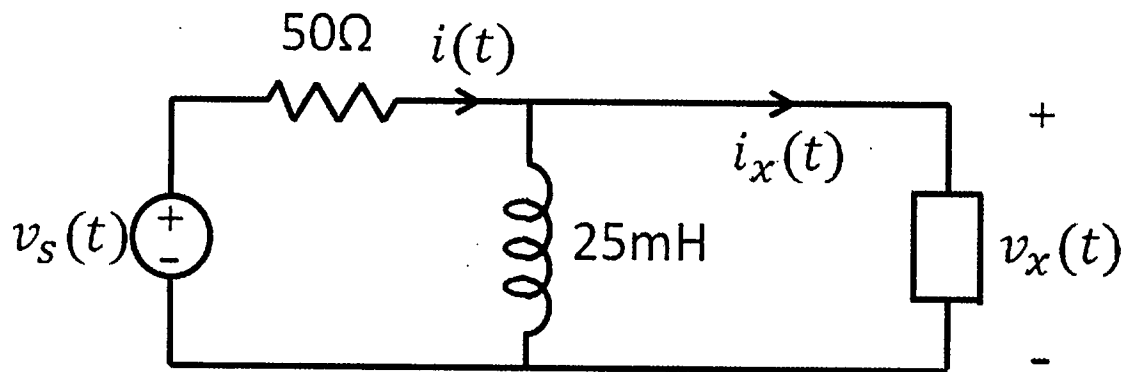Q5 continued. (Circuit diagram has been duplicated for your convenience)



(c) [1 mark] Determine the impedance of the elements in the rectangular box.

$Z_x =$

(d) [4 marks] If the elements in the rectangular box can be modeled as a resistor connected in parallel with a capacitor, find the values of the resistance and the capacitance.

$R =$

$C =$

