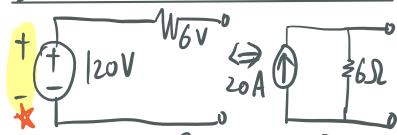


# Superposition & Linearity

→ You must include dependent sources!

Source Transformation:




Voltage & Current Division



$$V_{R_1} = V \cdot \frac{R_1}{R_1 + R_2}$$

$$V_R = V \cdot \frac{R_x}{\sum R_j}$$

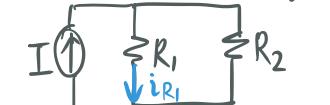

$$2R_1 = I \frac{R_1 + R_2}{R_1}$$

$$2R = I \cdot \frac{R_{eq}}{R_R}$$

Thevenin's Resistance

Find  $R_{TH} = R_N$ :

① Indep Sources:  $\oplus \rightarrow | \quad \ominus \rightarrow \circ$


② Only dep Sources:

• Apply Indep Sources at terminal Ohm's Law  
 $\oplus R_{TH} = \frac{IV}{I_{find}}$     $\ominus R_{TH} = \frac{V_{find}}{I}$


③ Both Indep & Dep:

$$R_{TH} = \frac{V_{DC}}{I_{SC}}$$

Thevenin's

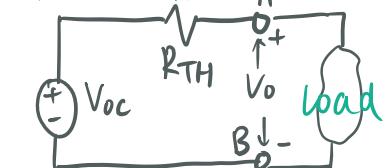

Norton's

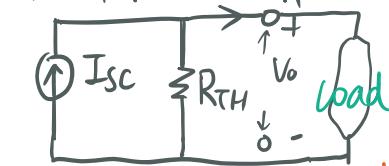

Look for Short Circuits!

Maximum Power Transfer

$$P_L = i^2 R_L = \left( \frac{V}{R_{TH} + R_L} \right)^2 R_L$$



## DC Analysis: L & C

Capacitors: first

$$i(t) = C \frac{dv}{dt}$$

$i=0$  in DC Analysis (open C)

$$v(t) = V(t_0) + \frac{1}{C} \int_{t_0}^t i(x) dx$$

$$P = VI = CV \frac{dv}{dt}$$

$$W_C = \frac{q^2}{2C} = \frac{1}{2} CV^2$$

Series:  $\frac{1}{C_{tot}} = \sum \frac{1}{C_j}$  Parallel:  $C_{tot} = \sum C_j$

(Q same, DV add)  $\Delta V$  same, Q add

Inductors:

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(x) dx$$

$$v(t) = L \frac{di}{dt}$$

$$P = VI = (L \frac{di}{dt}) I(t)$$

$$W_L = \frac{1}{2} L I^2$$

Series:  $L_{tot} = \sum L_j$  Parallel:  $\frac{1}{L_{tot}} = \sum \frac{1}{L_j}$

## First Order Circuits

Step-by-step Approach:

$$1. X(t) = k_1 + k_2 e^{-\frac{t}{T}}$$

$$2. \text{Find } X(0^-) \text{ & } X(0^+)$$

$$3. \text{Find } X(\infty)$$

$$T = R_{TH} \cdot C$$

$$I = L / R_{TH}$$

$$4. X(t) = X(\infty) + [X(0^+) - X(\infty)] e^{-\frac{t}{T}}$$

## Sinusoids

General form:

$$x(t) = X_M \sin(\omega t)$$

, where  $\omega = \frac{2\pi}{T} = 2\pi f$   
 $T$  [=sec]  $f$  [= #cycles/sec]

$$x(w(t+T)) = x(wt)$$

$$\sin(\omega t)$$

$$\sin(\omega t + \theta)$$

lags by  $\theta$  radians

$$\cos(\omega t) = \sin(\omega t + 90^\circ)$$

$$\sin(\omega t) = \cos(\omega t - 90^\circ)$$

$$-\cos(\omega t) = \cos(\omega t \pm 180^\circ)$$

$$-\sin(\omega t) = \sin(\omega t \pm 180^\circ)$$

$$\sin(\alpha + \beta) = \sin \alpha \cos \beta + \cos \alpha \sin \beta$$

$$\cos(\alpha + \beta) = \cos \alpha \cos \beta - \sin \alpha \sin \beta$$

$$\sin(\alpha - \beta) = \sin \alpha \cos \beta - \cos \alpha \sin \beta$$

$$\cos(\alpha - \beta) = \cos \alpha \cos \beta + \sin \alpha \sin \beta$$

$$\text{Reactive component}$$

Positive j → inductors

Negative j → capacitors

Negative R → check math

Short Circuit



Open Circuit



$$R: Z = R$$

$$L: Z = j\omega L$$

$$C: Z = \frac{1}{j\omega C}, \frac{-1}{\omega C}$$

Series:  $Z_{tot} = Z_1 + Z_2 \dots$  Parallel:  $\frac{1}{Z_{tot}} = \sum \frac{1}{Z_j}$

Inductance (L): Set =  $j\omega L$   
 Capacitance (C): Values =  $\frac{1}{j\omega C}$

Power in AC Circuit  
 $P_L = P_C = 0$

Admittance:

$$Y = \frac{1}{Z} = \frac{I}{V} [S]$$

$$Y = G + jB$$

conductance Susceptance.

Other formulas:

Circle:  $S = r\theta$ ,  $\theta$  = radians

$$\text{Sphere } V = \frac{4}{3} \pi r^3$$

$$SA = 4\pi r^2$$

Proton mass = neutron mass

$$1.67 \times 10^{-27} \text{ kg}$$

Electron mass:

$$9.11 \times 10^{-31} \text{ kg}$$

Boltzmann's Constant:

$$k_B = 1.38 \times 10^{-23} \text{ J/K}$$

Electron Charge magnitude:

$$e = 1.60 \times 10^{-19} \text{ C}$$

Electron Volt

$$1 \text{ eV} = 1.60 \times 10^{-19} \text{ J}$$

Speed of Light

$$c = 3 \times 10^8 \text{ m/s}$$

Universal gravitational constant

$$G = 6.67 \times 10^{-11} \frac{\text{N} \cdot \text{m}^2}{\text{kg}^2}$$

$$\epsilon_0 = 8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}}$$




$$K = 1/4\pi\epsilon_0 = 9 \times 10^9 \text{ N} \cdot \text{m}^2/\text{C}^2$$

$$u_0 = 4\pi \times 10^{-7} \text{ T} \cdot \text{m} / \text{A}$$

Magnetic Constant

$$k' = \frac{\mu_0}{4\pi} = 1 \times 10^{-7} \frac{\text{T} \cdot \text{m}}{\text{A}}$$
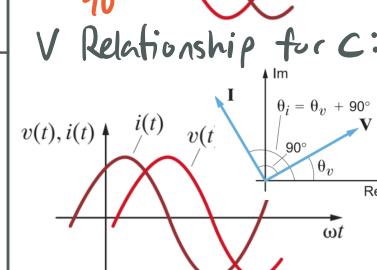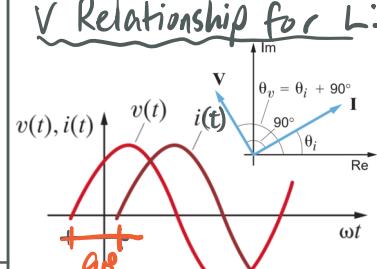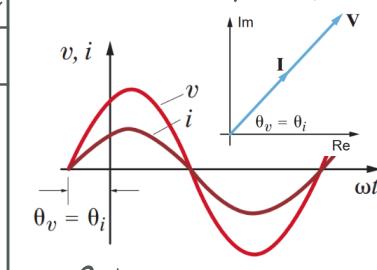
$$1 \text{ atm} = 10^5 \frac{\text{N}}{\text{m}^2} = 10^5 \text{ Pa}$$



$$\text{Phasors } R: V = RI$$

$$L: V = j\omega L I$$

$$C: V = \frac{1}{j\omega C} I$$

## Impedance

$$Z = \frac{V}{I} [\Omega]$$

Impedance is not a phasor!

$$= R + jX$$

Resistive Component      Reactive Component

$$j = -1/j$$

## Electric Potential

$$V = \frac{-W\alpha}{q_0} = \frac{U}{q_0}$$

$W_{\text{el}} = \text{Work done by electric force.}$

## Electric Potential Energy

$$U = qV \quad (\text{place } q \text{ at } V)$$

$$\text{Uniform } \vec{E}: \Delta V = -E \Delta X$$

$$\Delta U = q \Delta V = q(V_f - V_i)$$


Potential Due to a charged  $q$

$$V = \frac{kq}{r}$$

$$V_{\text{tot}} = k \sum \frac{q_i}{r_i}$$

Potential Energy & Density
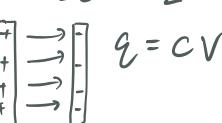
$$U = \frac{q^2}{2C} = \frac{CV^2}{2} \quad u = \frac{\epsilon_0 E^2}{2}$$



## Current:

$$i = \int \vec{J} \cdot d\vec{A} \quad i = \frac{dq}{dt}$$

## Mechanical Energy:

$$\Delta K = -q \Delta V$$

$$\Delta K = -q \Delta V + W_{\text{app}}$$

$$\vec{F} = q \vec{E} \quad q \Delta V$$

## Summary of Gauss's Law

$$\text{Surface of Charged conductor } E = \frac{0}{\epsilon_0}$$

$$\text{Line of charge: } E = \frac{\lambda}{2\pi\epsilon_0 r}$$

$$\infty \text{ non-conducting sheet } E = \frac{0}{2\epsilon_0}$$

$$\text{outside a spherical shell of Charge } E = \frac{kq}{r^2}$$

$$\text{Inside a uniform spherical shell } E = 0$$

$$\text{Inside uniform sphere of charge } E = \left( \frac{q}{4\pi\epsilon_0 R^3} \right) r$$

## Capacitors:

$$\parallel \text{ capacitor } C = \frac{\epsilon_0 A}{d}$$

$$\text{cylindrical capacitor } C = 2\pi\epsilon_0 \frac{L}{\ln(b/a)}$$



Spherical Capacitor with concentric spherical plate  $C = 4\pi\epsilon_0 \frac{ab}{b-a}$

Isolated Sphere  $C = 4\pi\epsilon_0 R$

$$\Delta V = - \int_i^f \vec{E} \cdot d\vec{s}$$

Insert Dielectric to  $C$

$\propto$  remains  $C' = KC$

## Drift speed

$$\vec{J} \left[ \frac{A}{m^2} \right] = (n e) \vec{V}_d$$

$n e$  = carrier charge density

$$n = \frac{\text{charge carrier}}{\text{unit volume}}$$

## Resistivity

$$\rho [\Omega m] = \frac{1}{\sigma} = \frac{E}{J}$$

$$\vec{E} = \rho \vec{J}$$

Resistance of wire:

$$R = \frac{\rho L}{A}$$

Change of  $\rho$  with temperature

$$\rho - \rho_0 = \rho_0 \alpha (T - T_0)$$

$\rho_0$  = resistivity at  $T_0$

$\alpha$  = temperature coefficient of resistivity for material

## Magnetic field:

$$\vec{F}_B = q \vec{V} \times \vec{B}$$

$$B [= T]$$

## Ampere's Law:

$$\oint \vec{B} \cdot d\vec{s} = \mu_0 i_{\text{enc}}$$

## Biot Savart Law:

$$d\vec{B} = \frac{\mu_0}{4\pi} \frac{i d\vec{s} \times \hat{r}}{r^2}$$

Long straight wire  $\vec{B}$

$$\text{outside } B = \frac{\mu_0 i}{2\pi r}$$

$$\text{inside } B = \left( \frac{\mu_0 i}{2\pi r^2} \right) r$$

$r$  = radius of wire.

## ideal solenoid:

$$B = \mu_0 i N$$

## Parallel current

$$F_{ba} = \frac{\mu_0 L i_a i_b}{2\pi d}$$

Straight wire:

$$\vec{F}_B = i L \vec{X} \vec{B}$$

$$d\vec{F}_B = i dL \vec{X} \vec{B}$$

Power of wire

Derivation

$$|E| = \frac{d\Phi_B}{dt} = \frac{d}{dt} BLx$$

$$= BL \frac{dx}{dt} = BLV$$

$$i = \frac{BLV}{R}$$

$$P = FV = \frac{B^2 L^2 V^2}{R}$$

$$F_B = ILB \quad \mathcal{E} = |BLV|$$

Thermal Energy Rate:

$$P = \left( \frac{BLV}{R} \right)^2 = \frac{B^2 L^2 V^2}{R}$$

## Circular Arc $\vec{B}$

$$B = \frac{\mu_0 i \phi}{4\pi R}$$

$\phi$  = angle in radians

## Power:

$$P = iV = i^2 R = \frac{V^2}{R} \quad (\text{resistive dissipation})$$

## Magnetic flux $\Phi$

$$\Phi_B = \int \vec{B} \cdot d\vec{A}$$

$$\Phi_B = BA \quad (B \perp to A) \quad (B \text{ uniform})$$

## Faraday's Law of Induction

$$\mathcal{E} = -\frac{d\Phi_B}{dt}$$

Coil of  $N$  turns:

$$\mathcal{E} = -N \cdot \frac{d\Phi_B}{dt}$$

## Lenz's Law

Induced emf will either oppose / same direction depending on magnetic flux. Self induction

$$\mathcal{E}_L = -L \cdot \frac{di}{dt}$$

## Inductance

$$L = \mu_0 n^2 A l$$

Inductor w/  $N$  loops

$$L = \frac{N \Phi_B}{i}$$

## Magnetic Energy

$L$  with  $i$

$$UB = \frac{1}{2} L i^2$$

$$\frac{\mu_0 N^2 A}{l} = \mu_0 n^2 l A$$

$l$  = solenoid's length

$N$  = num of turns

Supply & absorb





Supply  $\rightarrow$  pump from low to high

absorb  $\rightarrow$  vice versa

## Circuit Analysis Special Cases:

- choose ground
- Analyse each KVL or KCL individually.
- write down unknowns / what values it can solve for.
- Go for 1 unknown first

\* Direction of current is important!

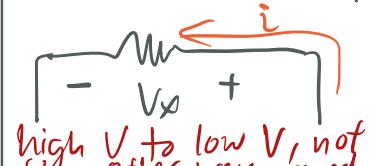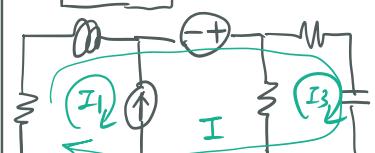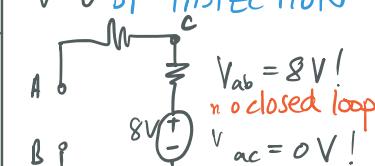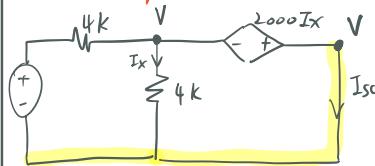

High  $V$  to low  $V$ , not the other way around