

UNIVERSITY OF TORONTO
FACULTY OF APPLIED SCIENCE AND ENGINEERING

ECE 110H1 S -- ELECTRICAL FUNDAMENTALS
FINAL EXAMINATION, APRIL 18, 2012

First Year -- Computer, Electrical, Industrial, Mechanical, Materials,
and Track One Engineering Programs.

Examiners – B. Bardakjian, P. Herman, M. Mojahedi, H. Timorabadi and B. Wang

NAME : (PLEASE PRINT)	Family Name	Given Name
STUDENT NUMBER :		

EXAMINATION TYPE C : One 8 ½ “ x 11” (double-sided) aid sheet allowed

CALCULATORS : Non-programmable type (as specified in the Faculty Calendar) allowed

DURATION : 2.5 hours


- INSTRUCTIONS :
- DO NOT UNSTAPLE THIS EXAMINATION BOOK.
 - Answer all six questions.
 - All work is to be done on these pages. Show steps, compute numerical results when requested and state units.
 - You may use the back of the preceding page for rough work.

Question	Mark
1	
2	
3	
4	
5	
6	
Total	

1. [15 marks] Circle the best answer in the following questions. [1.5 marks per question].


- a) Two charged particles are fixed in place as shown in the figure. Determine in which region on the line a proton can be placed such that the proton remains at rest?

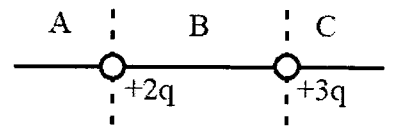- 1) region A
- 2) region B
- 3) region C



- b) Five charges are arranged at the corners and center of a square as shown below. What is the direction of the force on the center charge?

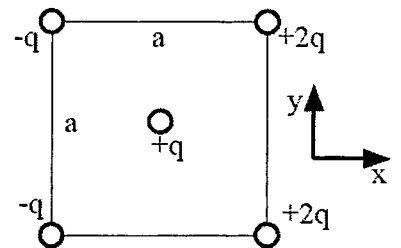- 1) positive x-direction
- 2) negative x-direction
- 3) positive y-direction
- 4) negative y-direction



- c) If a positively charged object is brought close to but not touching a conductor that is insulated from its surroundings then what is the total charge on the conductor?

- 1) positive
- 2) negative
- 3) zero
- 4) cannot determine

- d) Considering a large distance from the object, determine in which case an electric field (E) is not produced.

- 1) one stationary electron
- 2) one moving electron
- 3) a wire with an electric current flowing in it
- 4) a tiny triangle consisting of three equal charges (one negative and the others positive)


- e) In the following formula

$$\vec{F} = q\vec{v} \times \vec{B}$$

- 1) \vec{F} must be perpendicular to \vec{v} but not necessarily to \vec{B}
- 2) \vec{F} must be perpendicular to \vec{B} but not necessarily to \vec{v}
- 3) \vec{v} must be perpendicular to \vec{B} but not necessarily to \vec{F}
- 4) all three vectors must be mutually perpendicular
- 5) \vec{F} must be perpendicular to both \vec{v} and \vec{B}


- f) The figure shows the motion of electrons in a wire which is near the N pole of a magnet. The wire will be pushed

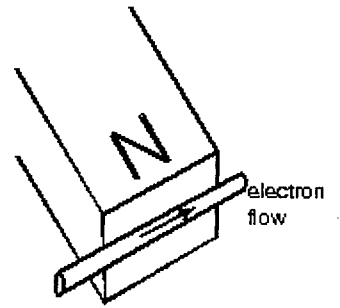- 1) toward the magnet
- 2) away from the magnet
- 3) downwards
- 4) upwards
- 5) along its length



- g) In the circuit shown, there will be a non-zero reading in the Ammeter (Galvanometer) G :

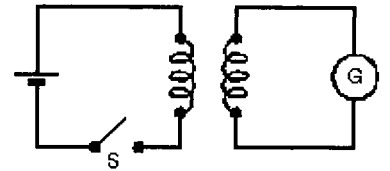- 1) only just after S is closed
- 2) only just after S is opened
- 3) only while S is kept closed
- 4) never
- 5) only just after S is opened or closed




- h) If 500 J of work is required to carry a 40 C charge from one point to another, the potential difference between these two points is:

- 1) 12.5 V
- 2) $20,000\text{ V}$
- 3) 0.08 V
- 4) depends on the path
- 5) none of above

- i) To charge a 1 F capacitor with 2 C requires a potential difference of:

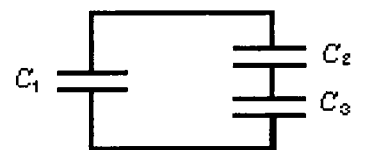- 1) 2 V
- 2) 0.2 V
- 3) 5 V
- 4) 0.5 V
- 5) none of above

- j) Capacitor C_1 is connected alone to a battery initially and charged until the magnitude of the charge on each plate is $4.0 \times 10^{-8}\text{ C}$. Then it is removed from the battery and connected to two other capacitors C_2 and C_3 , as shown in the figure below. The charge on the positive plate of C_1 is then $1.0 \times 10^{-8}\text{ C}$. The charges on the positive plates of C_2 and C_3 are:






- 1) $q_2 = 3.0 \times 10^{-8}\text{ C}$ and $q_3 = 3.0 \times 10^{-8}\text{ C}$
- 2) $q_2 = 2.0 \times 10^{-8}\text{ C}$ and $q_3 = 2.0 \times 10^{-8}\text{ C}$
- 3) $q_2 = 5.0 \times 10^{-8}\text{ C}$ and $q_3 = 1.0 \times 10^{-8}\text{ C}$
- 4) $q_2 = 3.0 \times 10^{-8}\text{ C}$ and $q_3 = 1.0 \times 10^{-8}\text{ C}$
- 5) $q_2 = 1.0 \times 10^{-8}\text{ C}$ and $q_3 = 3.0 \times 10^{-8}\text{ C}$

2. [5 marks] A uniform magnetic field (B) in the direction out of the page, changes in time (t) as illustrated in the B - t diagram below. As a consequence, a charge (q) flows in a conducting circular loop according to the q - t diagram below.


Determine:

- Direction of current in the circular conductor. Justify. [1 mark]
- Resistance in the circular conductor. [4 marks]

Conducting Loop

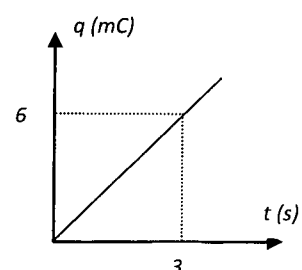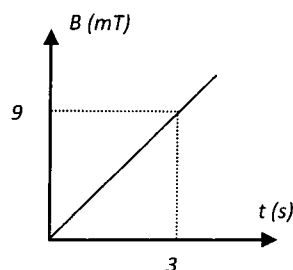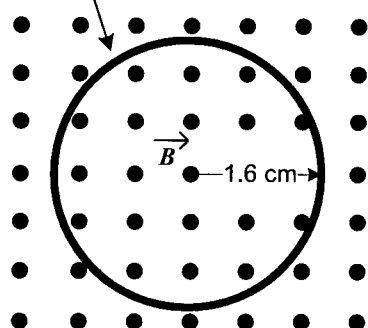


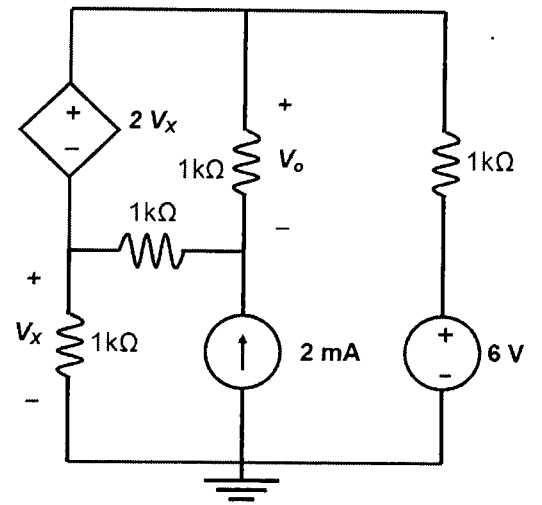3. [10 marks] Find the voltage V_0 in the circuit shown.




4. [10 marks] For the circuit shown:

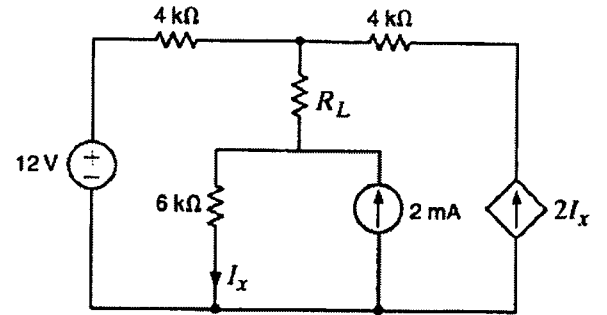a) Find the Thévenin equivalent circuit as seen by load R_L . [8 marks]



b) Optimize R_L for maximum power transfer from the circuit and calculate the power dissipated in R_L . [2 marks]

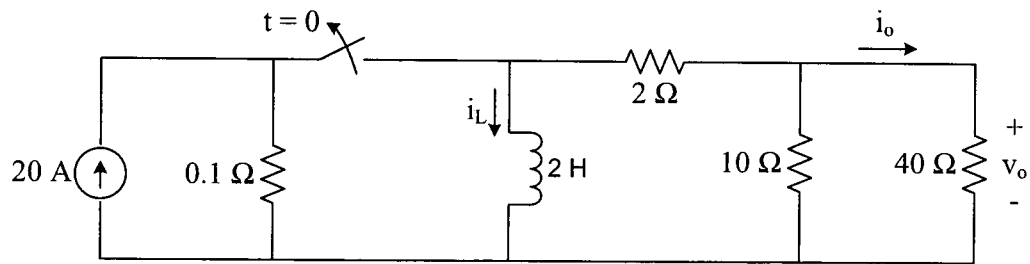5. [10 marks] The switch in the circuit shown below has been closed for a long time before it is opened at $t = 0$.



a) Determine $i_L(t)$ for $t > 0$. [4 marks]

b) Find $i_o(t)$ for $t > 0$. [2 marks]


c) What is the energy stored in the inductor just before the switch opens. [1 mark]

d) What percentage of that energy is dissipated in the $10\ \Omega$ resistor a long time after the switch is opened. [3 marks]

6. [10 marks]

Part a) For the AC circuit shown below, $v_s(t) = 20 \sin(10^6 t + 125^\circ) \text{ V}$.

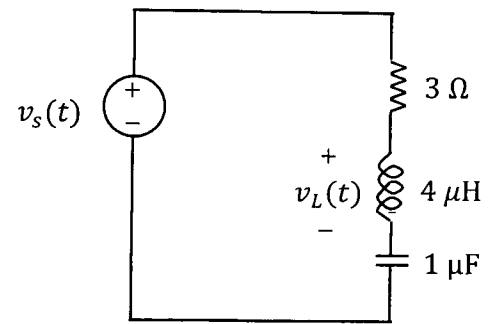
i) Redraw the circuit in the frequency domain and indicate the corresponding values of the phasor and the impedances. [3 marks]



ii) Determine the voltage across the inductor, $v_L(t)$. [2 marks]

Part b) For the circuit shown below, the frequency is 1 MHz.

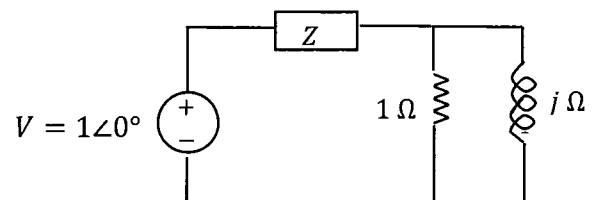i) Determine the value of the impedance Z if the impedance seen by the source is purely real and equal to 1Ω ? [2 marks]



ii) How do you build such an impedance Z using circuit components? What are the values of those components? [3 marks]