

ECE110 - Quiz #4

Only non-programmable calculators are allowed.

Duration: 30 Minutes

First Name: _____ Last Name: _____

Student #: _____ Tutorial Section: _____

In the circuit shown below apply Nodal Analysis to determine:

- a) Voltage at nodes b and c . [2 Marks]
- b) Currents I_X , I_Y , and I_Z . [2 Marks]
- c) Power by current source. [1 Mark]

