

## ECE110 - Quiz #4

Only non-programmable calculators are allowed.

Duration: 45 Minutes


First Name: \_\_\_\_\_ Last Name: \_\_\_\_\_

Student #: \_\_\_\_\_ Tutorial Room: \_\_\_\_\_

**Q1** [3 Marks] Clearly circle the correct answer.

- i. What is the equivalent resistance seen from nodes **a** and **b** in the following circuit?

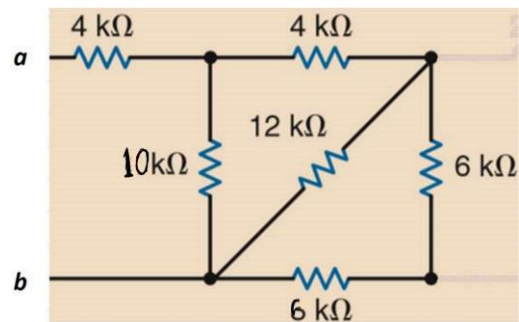
- a) 12 k $\Omega$
- b) 11 k $\Omega$
- c) 10 k $\Omega$
- d) 9 k $\Omega$
- e) None of the above.



**Answer: d**

- ii. In the following circuit, what is the equivalent resistance seen by the current source?

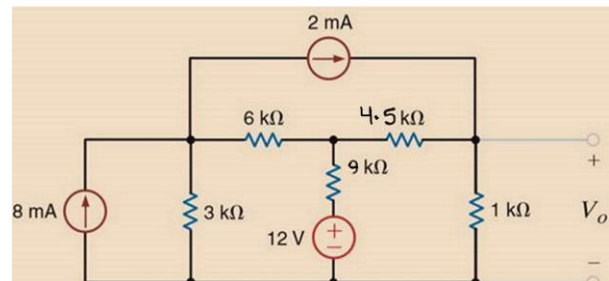
- a) 800  $\Omega$
- b) 900  $\Omega$
- c) 1000  $\Omega$
- d) 999  $\Omega$
- e) None of the above.



**Answer: b**

- iii. How many nodes are in the following circuit?

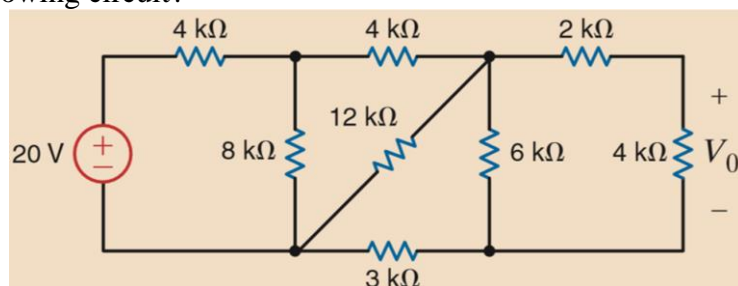- a) 5
- b) 6
- c) 7
- d) 8
- e) None of the above.




**Answer: b**

**Q2** [7 Marks] In the circuit shown below apply Nodal Analysis to determine:

a) Voltages at nodes  $V_1$ ,  $V_2$ , and  $V_3$ . [3.5 Marks]

b) Current  $2V_x$ . [1 Mark]

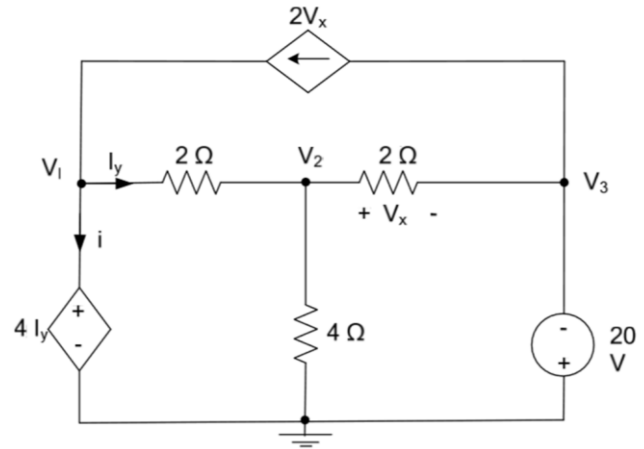c) Power by dependent voltage source. Is this power absorbed or supplied? [2.5 Mark]



Part a)

$$V_3 = -20 \text{ (V)}$$

$$\left\{ \begin{array}{l} V_1 = 4I_y \\ I_y = \frac{V_1 - V_2}{2} \end{array} \right\} \Rightarrow V_1 = 2V_1 - 2V_2 \Rightarrow V_1 - 2V_2 = 0 \quad (1)$$

Apply KCL @ Node  $V_2$   $\sum I_{\text{leaving}} = 0$

$$\Rightarrow \frac{V_2 - V_1}{2} + \frac{V_2 - V_3}{2} + \frac{V_2}{4} = 0$$

$$\text{times 4} \Rightarrow -\frac{1}{2}V_1 + V_2\left(\frac{1}{2} + \frac{1}{2} + \frac{1}{4}\right) = \frac{V_3}{2}$$

$$\begin{array}{l} -2V_1 + V_2(2+2+1) = 2V_3 \\ \left\{ \begin{array}{l} -2V_1 + 5V_2 = -40 \quad (2) \\ V_1 - 2V_2 = 0 \quad (1) \end{array} \right\} \Rightarrow \left\{ \begin{array}{l} -2V_1 + 5V_2 = -40 \\ 2V_1 - 4V_2 = 0 \end{array} \right. \\ \hline V_2 = -40 \text{ (V)} \\ \rightarrow V_1 = 2V_2 = 2(-40) \Rightarrow V_1 = -80 \text{ (V)} \end{array}$$

Free

Part b)

$$V_X = V_2 - V_3 = -40 - (-20) = -20 \text{ (V)}$$

$$\Rightarrow 2V_X = 2(-20) = -40 \text{ (A)}$$

Part c)  $P = VI \Rightarrow P = (4I_Y)(i)$

Need  $I_Y$  and  $i$

$$I_Y = \frac{V_1 - V_2}{2} = \frac{-80 - (-40)}{2} = \frac{-40}{2} = -20 \text{ (A)}$$

Apply KCL @ Node  $V_1$

$$2V_X = i' + I_Y \Rightarrow i' = 2V_X - I_Y$$

$$i' = (-40) - (-20) = -20 \text{ (A)}$$

$$P = 4(-20)(-20) = 1600 \text{ (w/ Absorbing)}$$