
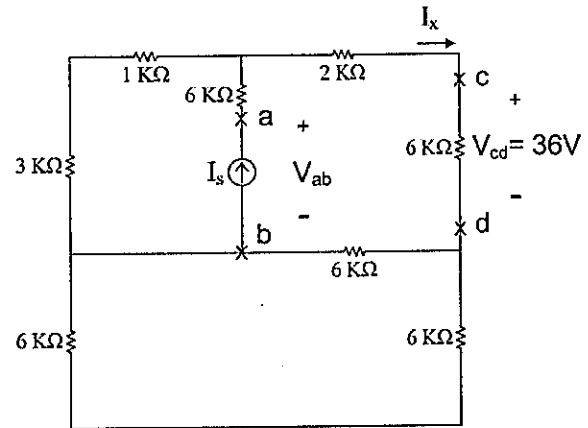


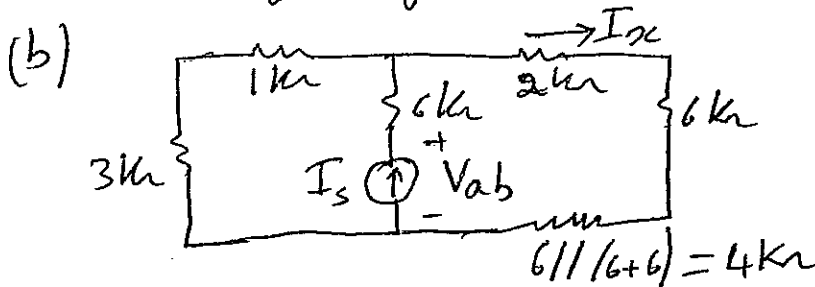1. [10 marks] For the circuit shown below, use circuit reduction, voltage division, current division, KCL, KVL and Ohm's law to calculate:

- Current  $I_x$ . (1 mark)
- Current  $I_s$ . (4 marks) (*Hint: You may need to simplify the circuit first*)
- Voltage  $V_{ab}$ . (3 marks)
- $R_{ab}$ , the equivalent resistance between the two points a and b seen by the current source. (2 marks)



$$(a) I_x = \frac{V_{cd}}{6} = \frac{36}{6} = 6 \text{ mA}$$




By Current division :  $I_x = I_s \frac{4}{4+2+6+4}$  so  $I_s = 4I_x = 24 \text{ mA}$

$$(c) V_{ab} = 6I_s + (2+6+4)I_x = 6I_s + 12I_x = 216 \text{ V}$$

By KVL

$$(d) R_{ab} = \frac{V_{ab}}{I_s} = \frac{216}{24} = 9 \text{ k}\Omega$$

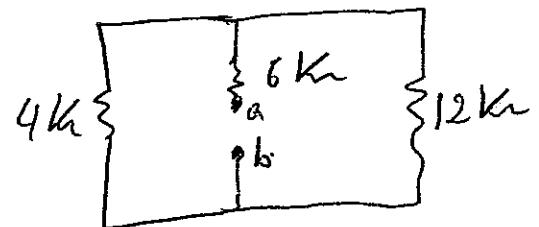
$$\underline{\underline{or}} \quad R_{ab} = 6 + (4 \parallel 12) = 9 \text{ k}\Omega$$



2. [10 marks] For the circuit shown where  $V_s$ ,  $k$ ,  $R_1$ ,  $R_2$  and  $R_3$  are constants:

(a) Write the equations for nodal analysis. (5 marks)

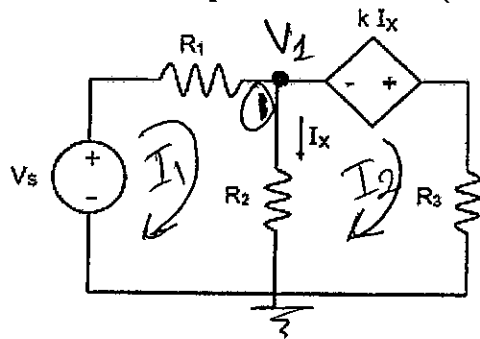(b) Write the equations for mesh (loop) analysis. (5 marks)



$$(a) \quad \frac{V_1 - V_s}{R_1} + \frac{V_1}{R_2} + \frac{V_1 + k I_x}{R_3} = 0 \quad (\text{KCL at node } \textcircled{1})$$

$$I_x = \frac{V_1}{R_2} \quad (\text{Dependent variable equation})$$



$$(b) \quad -V_s + I_1 R_1 + (I_1 - I_2) R_2 = 0 \quad (\text{KVL}_1)$$

$$-k I_x + I_2 R_3 + (I_2 - I_1) R_2 = 0 \quad (\text{KVL}_2)$$

$$I_x = I_1 - I_2 \quad (\text{Dependent variable equation})$$

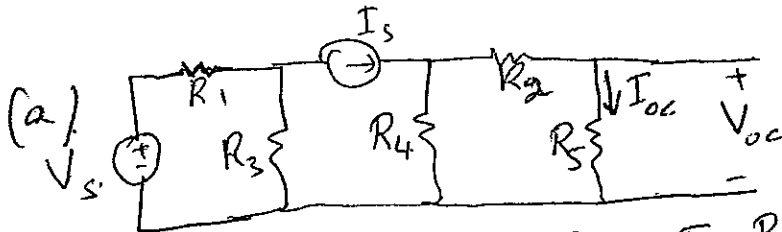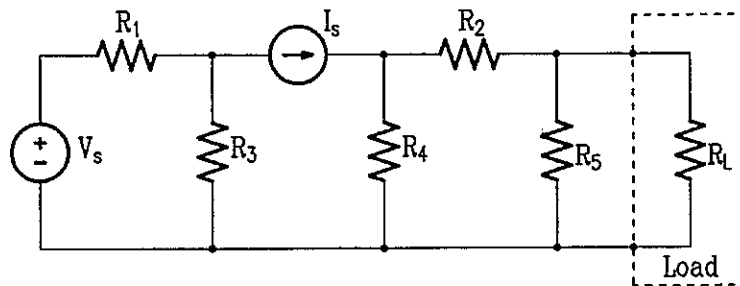3. [10 marks] Consider the circuit below. Known parameters are:  $R_1 = 50 \Omega$ ,  $R_2 = 20 \Omega$ ,  $R_3 = 50 \Omega$ ,  $R_4 = 100 \Omega$ ,  $R_5 = 80 \Omega$ ,  $V_s = 20 \text{ V}$ , and  $I_s = 20 \text{ A}$ . Determine the following:


- Thevenin equivalent voltage seen by the load. (4 marks)
- Thevenin equivalent resistance seen by the load. (3 marks)
- What is the power transferred to the load, if the load resistance is  $R_L = 32 \Omega$ . (3 marks)



By current division  $I_{oc} = \frac{I_s R_4}{R_4 + R_2 + R_5} = 20 \frac{100}{100 + 20 + 80} = 10 \text{ A}$


so  $V_{th} = V_{oc} = I_{oc} R_5 = (10)(80) = 800 \text{ V}$

(b)

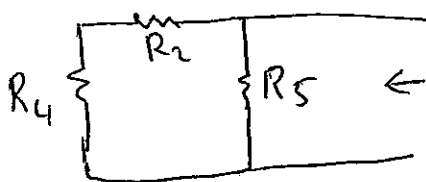

$R_{th} = R_5 // (R_2 + R_4) = \frac{(80)(120)}{80 + 120} = \frac{(80)(120)}{200} = 48 \Omega$

(c)

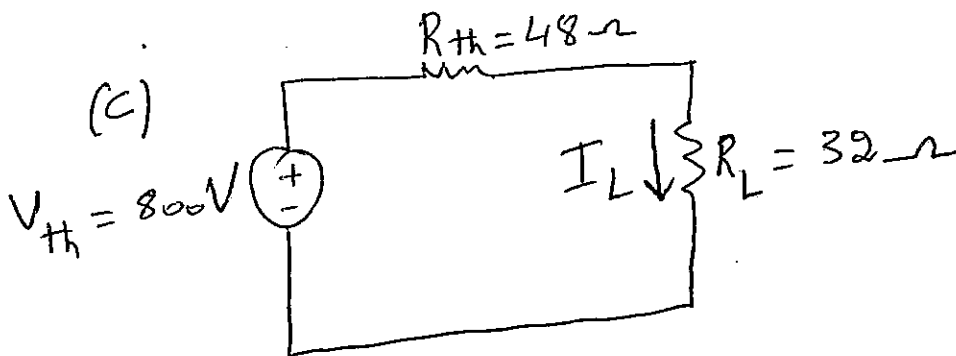

$I_L = \frac{V_{th}}{R_{th} + R_L} = \frac{800}{48 + 32} = 10 \text{ A}$

$P_L = I_L^2 R_L = (10)^2 (32) = 3200 \text{ W}$