



First name (please write as legibly as possible within the boxes)

[illegible]

Last name

[illegible]

Student ID number

[illegible]



749B4F16-2CB0-4DA3-B629-9D29484005E5

final-exam-bl0e3

#710 Page 2 of 12

University of Toronto
Faculty of Applied Science and Engineering
Department of Electrical and Computer Engineering

ECE110H1S – Electrical Fundamentals
Final Examination – April 24, 2023, 6:30 pm

$$(e = 1.6 \times 10^{-19} \text{ C}, \epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}, \mu_0 = 4\pi \times 10^{-7} \text{ H/m}, g = 9.81 \text{ N/kg})$$

Examination Type: C (Students may use a single, double-sided 8.5" x 11" aid sheet, handwritten or printed)

Calculators: Non-programmable calculators (Casio FX-991MS & Sharp EL-520X) are allowed.

Duration: 2.5 hours

Instructions:

Answer all five questions.


For full marks, you must show methods, state UNITS and compute numerical answers (when requested).

There is two extra blank pages at the end for rough work.




Q1.1) The figure shows a uniform electric field. An electron has moved from position (i) to position (f). Let ΔV be the change in electrostatic potential of the electron and ΔU be the change in potential energy of the electron. Circle the correct answer: [2 marks]

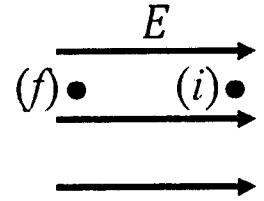- a) In moving from (i) to (f): $\Delta V < 0$ and $\Delta U < 0$
- b) In moving from (i) to (f): $\Delta V > 0$ and $\Delta U > 0$
- c) In moving from (i) to (f): $\Delta V < 0$ and $\Delta U > 0$
- d) In moving from (i) to (f): $\Delta V > 0$ and $\Delta U < 0$




1.2) The figure shows a positive volume charge density ρ_v (hatched region) completely enclosed by three spherical Gaussian surfaces S_1 , S_2 , and S_3 with radii R_1 , R_2 , and R_3 . Let Φ_1 , Φ_2 and Φ_3 be the electric fluxes through S_1 , S_2 , and S_3 , respectively. Circle the correct answer. [2 marks]

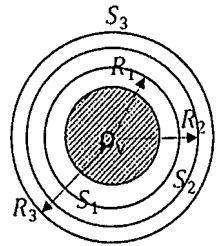- a) $\Phi_1 < \Phi_2 < \Phi_3$
- b) $\Phi_1 > \Phi_2 > \Phi_3$
- c) $\Phi_1 > \Phi_2 < \Phi_3$
- d) $\Phi_1 = \Phi_2 = \Phi_3$



1.3) The figure shows a uniform electric field and positive charge q^+ and negative charge q^- . What are the directions of the current densities associated with positive (\vec{J}^+) and negative charges (\vec{J}^-)? Circle the correct statement below: [2 marks]

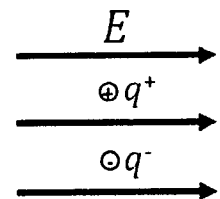- a) Both point from left to right
- b) Both point from right to left
- c) \vec{J}^+ points from left to right and \vec{J}^- points from right to left
- d) \vec{J}^+ points from right to left and \vec{J}^- points from left to right




1.4) In step 1, a capacitor was charged by connecting it to a battery. The battery was then removed. In step 2, a dielectric was inserted between the two plates of the same capacitor.

If the total electric field between the two plates of the capacitor in step-1 was \vec{E}_1 and the total electric field between the two plates of the capacitor in step-2 was \vec{E}_2 , circle the correct statement below. [2 marks]

- a) $|\vec{E}_1| > |\vec{E}_2|$
- b) $|\vec{E}_1| < |\vec{E}_2|$
- c) $|\vec{E}_1| = |\vec{E}_2|$
- d) $|\vec{E}_1| = |\vec{E}_2| = 0$

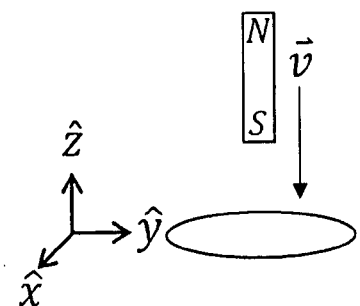1.5) The figure shows a bar magnet moving in the negative z-direction, toward a metallic ring placed in the x-y plane. On the figure, clearly indicate the direction of induced current. [2 marks]






D273788E-6037-4777-AAB8-1EB57368DF18

final-exam-b10e3


#710 Page 4 of 12

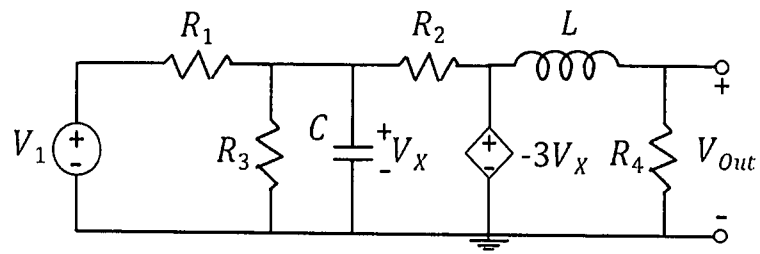Q2. Consider the following circuit where: $R_1 = 100 \, \Omega$, $R_3 = 100 \, \Omega$, $R_4 = 150 \, \Omega$, $C = 100 \text{ nF}$, $L = 5 \text{ mH}$. V_1 produces a DC voltage. Determine the value of R_2 that makes $V_{out}/V_1 = -1.2$.
[10 marks]





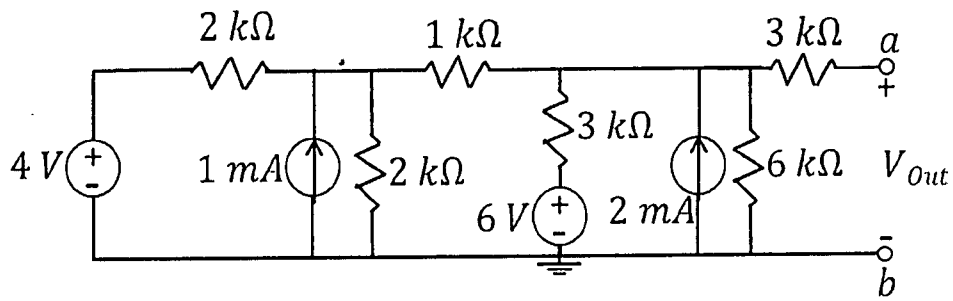Q3. A) Given the circuit below, find V_{out} using source transformation [7 marks].





1483DAEC-7817-4475-85A6-3BFF17D0D03A

final-exam-b10e3

#710 Page 6 of 12


Q3. B) If a load with resistance R_L is connected between the output terminals “a” and “b”, determine [3 marks]:

- (i) R_L for maximum power transfer
- (ii) The maximum power transferred.



Q4. The switch of the following circuit will open at $t = 0$ seconds.

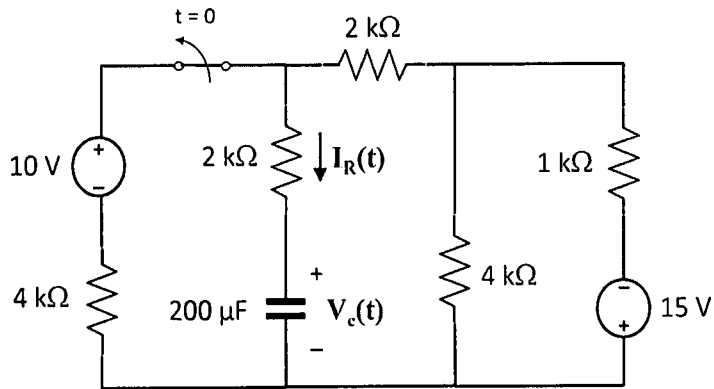A) Determine the expression for the voltage across the $200\ \mu\text{F}$ capacitor. Hint: use the step-by-step method [7 marks].






112FC62A-9556-47BF-89E3-160121475D03

final-exam-b10e3


#710 Page 8 of 12

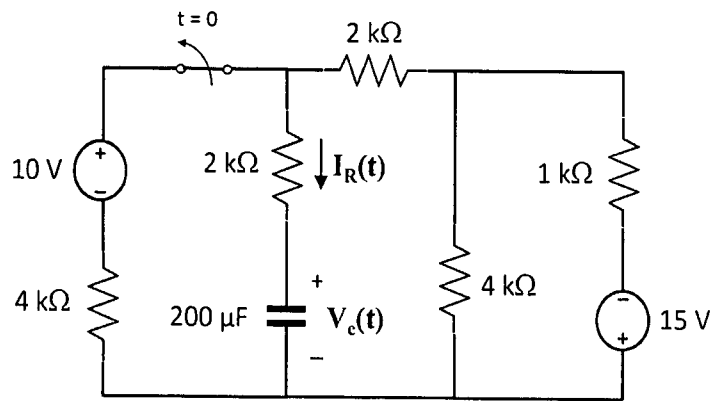B) Plot the current through the $2\text{ k}\Omega$ resistor [$I_R(t)$]. The circuit is reprinted for your convenience. [3 marks].





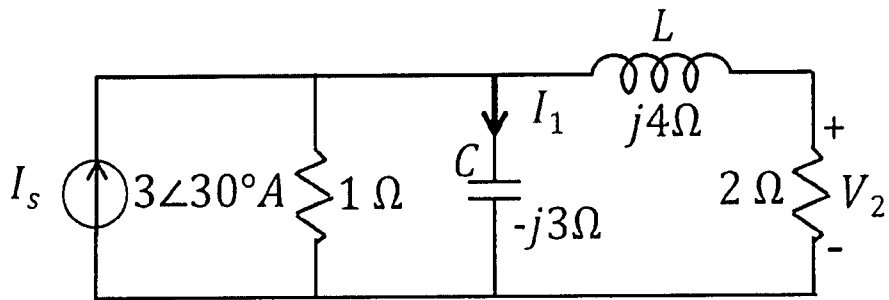Q5. The current source I_s in the circuit is a 60 Hz sinusoidal waveform.



A) Determine the current phasor, I_1 and the voltage phasor, V_2 . [4 marks]



6F26E026-E74F-4903-940D-883CDBB0C01D

final-exam-bl0e3

#710 Page 10 of 12

B) What is the voltage across the $2\ \Omega$ resistor, expressed as a function of time? Sketch the waveform. [2 marks]

C) Find the inductance, L , and the capacitance, C , in the circuit. [2 marks]

D) Suppose the frequency of the current source is doubled. Redraw the circuit and clearly indicate the impedance of each element. [2 marks]

F5F1E523-AA7E-482D-9A4C-9D9ACD7834D5

final-exam-b10e3

#710 Page 11 of 12





26DD5F85-8F00-48A9-AE5E-077DF1AD77C2

final-exam-b10e3

#710 Page 12 of 12