

UNIVERSITY OF TORONTO
FACULTY OF APPLIED SCIENCE AND ENGINEERING

ECE 110H1 S -- ELECTRICAL
FUNDAMENTALS FINAL EXAMINATION,
APRIL 18, 2018, 2:00 p.m.

First Year -- Computer, Electrical, Industrial, Mechanical, Materials,
and Track One Engineering Programs.

Examiners – B. Bardakjian, M. Mojahedi, B. Wang and P. Yoo

$$(e = 1.6 \times 10^{-19} \text{ C}, \epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}, \mu_0 = 4\pi \times 10^{-7} \text{ H/m}, g = 9.81 \text{ N/kg})$$

NAME :

(PLEASE PRINT)

Family (Last) Name

Given (First) Name

STUDENT NUMBER :

EXAMINATION TYPE : D (Students may use a single double sided 8.5" x 11" aid sheet)

CALCULATORS : \ Casio FX-991 (EX, EX Plus, or MS), Sharp EL-520 (X or W)

DURATION : 2.5 hours


- INSTRUCTIONS :
- Answer all five questions. Put the final answers in the boxes provided.
 - All work is to be done on these pages. Show steps, compute numerical results and state units. Write down any assumption made.
 - Please note that the exam papers are double-sided
 - **The last 2 blank pages may be removed for rough work.**

Question	Mark
1	
2	
3	
4	
5	
Total	

Q1 continued


1.4 (1 mark) An electron (e^-) in the presence of a uniform electric field \vec{E} moves from the initial position (i) to the final position (f). Let ΔU represent the change in potential energy and ΔV the change in electrostatic potential.

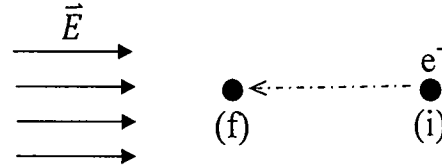- a. $\Delta U > 0$ and $\Delta V < 0$
- b. $\Delta U < 0$ and $\Delta V < 0$
- c. $\Delta U > 0$ and $\Delta V > 0$
- d. $\Delta U < 0$ and $\Delta V > 0$




1.5 (2 marks) Figure shows the cross section of two uniform sheets of positive charges placed at the right angle to each other. What angle do the equipotential surfaces make with the positive x -axis in the first quadrant (see figure)?

- a. 90°
- b. 0°
- c. 60°
- d. 135°

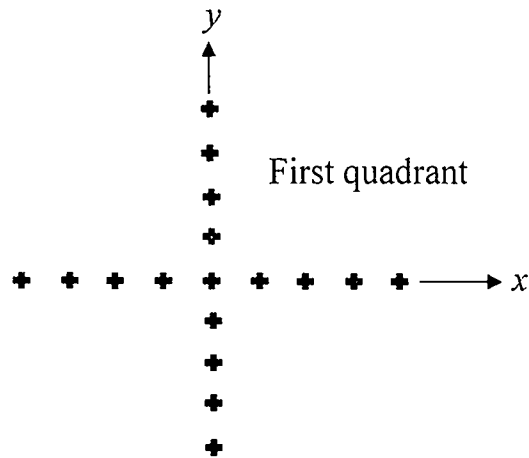

1.6 (1 mark) The voltage across a 2 [H] inductor is shown. What is the value of the current through the inductor at $t = 6$ [s]?

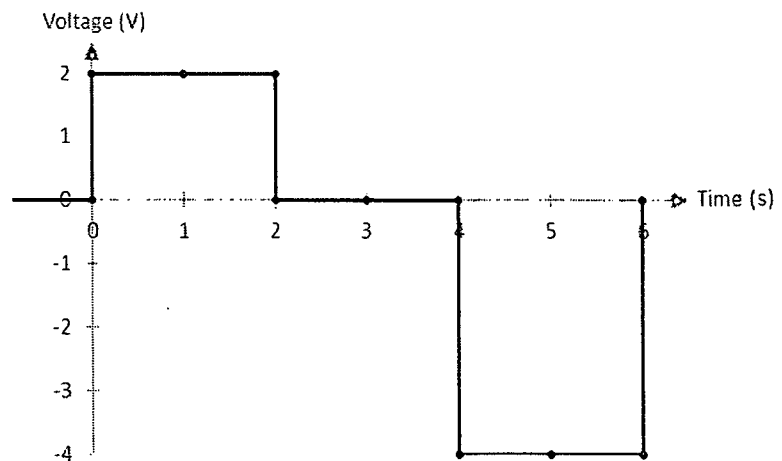
- a. 2 [A]
- b. -4 [A]
- c. 4 [A]
- d. -2 [A]



Q2 [10 marks]

Consider the following diagram where the two parts of the circuit are electromagnetically coupled by placing a coil inside a solenoid. The dimensions of the solenoid and coil are provided in the table below:

	Solenoid	Coil
Length (cm)	7	3
Diameter (mm)	5	2
Number of Turns	10,000	5,000

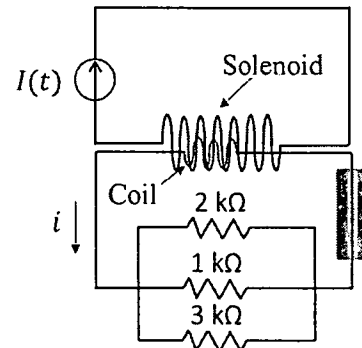


(a) (2 marks) For a current $I(t)$ applied by the independent current source, determine the magnitude of the electromotive force ($|\mathcal{E}|$) induced in the coil.

$|\mathcal{E}| =$

Q3 [10 marks]

Consider the following circuit:

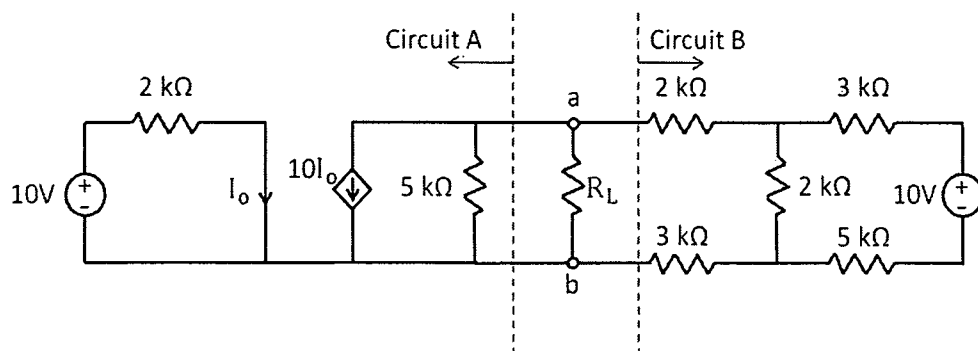


(a) (4 marks) Find the Thévenin equivalent of Circuit A between terminals a-b.

$$V_{th} =$$

$$R_{th} =$$

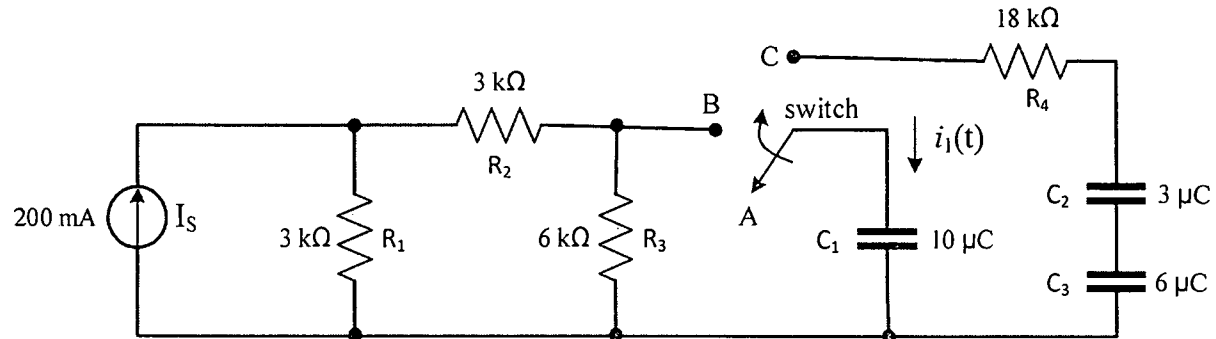Q4 [10 marks]

In the circuit shown below, the switch is initially at position A. At $t = 0$ s, the switch moves to position B. At $t = 5$ s, the switch moves to position C. Assume that all of the capacitors have zero stored energy at $t = 0$ s. Answer the following questions.



(a) (1 mark) Calculate the time constant of the circuit when the switch is in position B.


$\tau =$

(b) (2 marks) Calculate the voltage across the capacitor C_1 at $t = 1$ s.

$V_{C_1}(1) =$

Q5 [10 marks]

Consider the circuit shown:

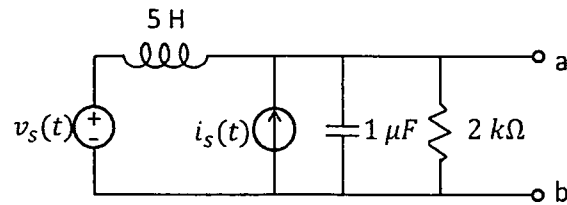

$$i_s(t) = 5 \cos(\omega t) \text{ mA.}$$

$$v_s(t) = 10 \cos(\omega t - 90^\circ) \text{ V}$$

(a) (7 marks) Compute the Thévenin equivalent circuit between terminals a & b for $\omega = 200 \text{ rad/s}$ in the frequency domain.

$V_{th} =$ $Z_{th} =$

THIS PAGE HAS BEEN LEFT INTENTIONALLY BLANK FOR SCRAP PAPER