

UNIVERSITY OF TORONTO  
FACULTY OF APPLIED SCIENCE AND ENGINEERING

FINAL EXAMINATION, APRIL 2005

First Year – Civil, Industrial, Mechanical and Materials Engineering Programs

ECE 110H1 S – ELECTRICAL FUNDAMENTALS

Exam. Type: A

Examiners – L. de Windt and B. Wang

NAME : (PLEASE PRINT)	FAMILY NAME	GIVEN NAME
STUDENT NUMBER :		

EXAMINATION TYPE : Type A – Paper for which no data are permitted other than the information printed on the examination paper.

CALCULATORS : ONLY Non-programmable scientific type allowed (models as specified in the Faculty Calendar).

DURATION : 2.5 hours

INSTRUCTIONS :

- DO NOT UNSTAPLE THIS EXAM. BOOK.
- Answer all ten questions.
- All ten questions are of equal weight.
- All work is to be done on these pages. Show methods, compute numerical results when requested and state units.
- Place your final answer in the corresponding box. You may use the back of the preceding page for rough work.

$e = 1.6 \times 10^{-19} \text{C}, \quad \epsilon_o = 8.85 \times 10^{-12} \text{ F/m}, \quad \mu_o = 4\pi \times 10^{-7} \text{ H/m}$
--

Question	Mark
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
Total	

Question 1 (10 marks)

Page 2 of 11

Six charges are equally spaced in a circle of radius 5m as shown in Figure 1. Determine the total electric field  $\vec{E}_T$ , at the center of the circle, due to the six charges.

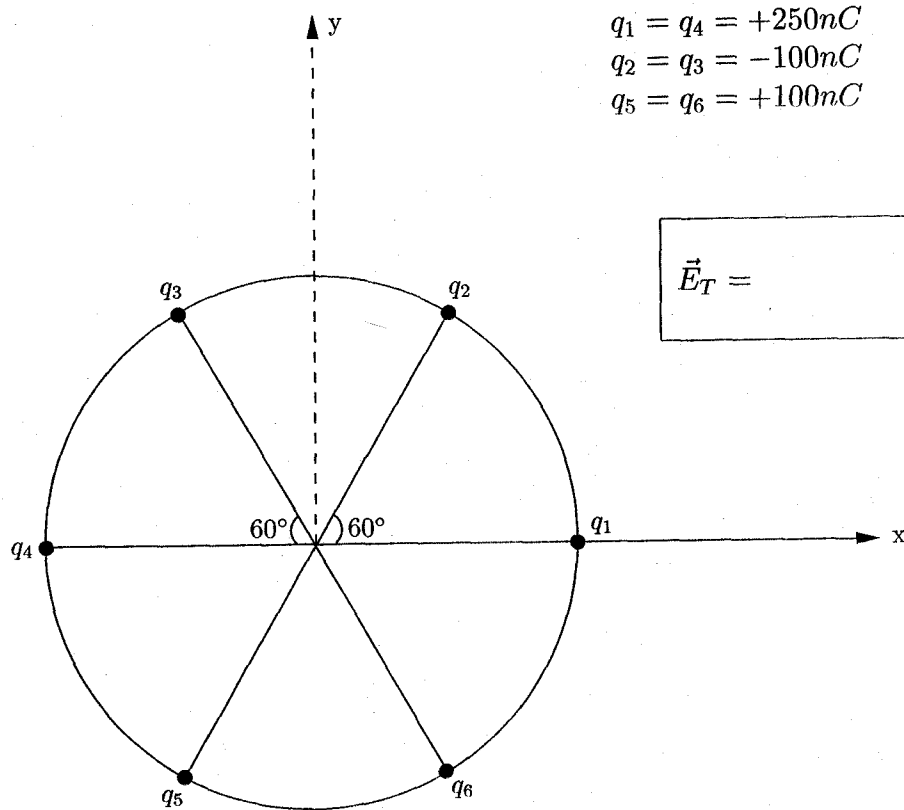


Figure 1

$$\begin{aligned} q_1 &= q_4 = +250nC \\ q_2 &= q_3 = -100nC \\ q_5 &= q_6 = +100nC \end{aligned}$$

$$\vec{E}_T =$$

Question 2 (10 marks)

Page 3 of 11

Two very long wires are located at  $(-1, 0)\text{m}$  and  $(1, 0)\text{m}$ . Wire #1 carries  $10\text{A}$  into the page and wire #2 carries  $10\text{A}$  out of the page as shown in Figure 2. Determine the total magnetic field  $\vec{B}_T$  due to both currents at the point  $(0, 1)\text{m}$ .

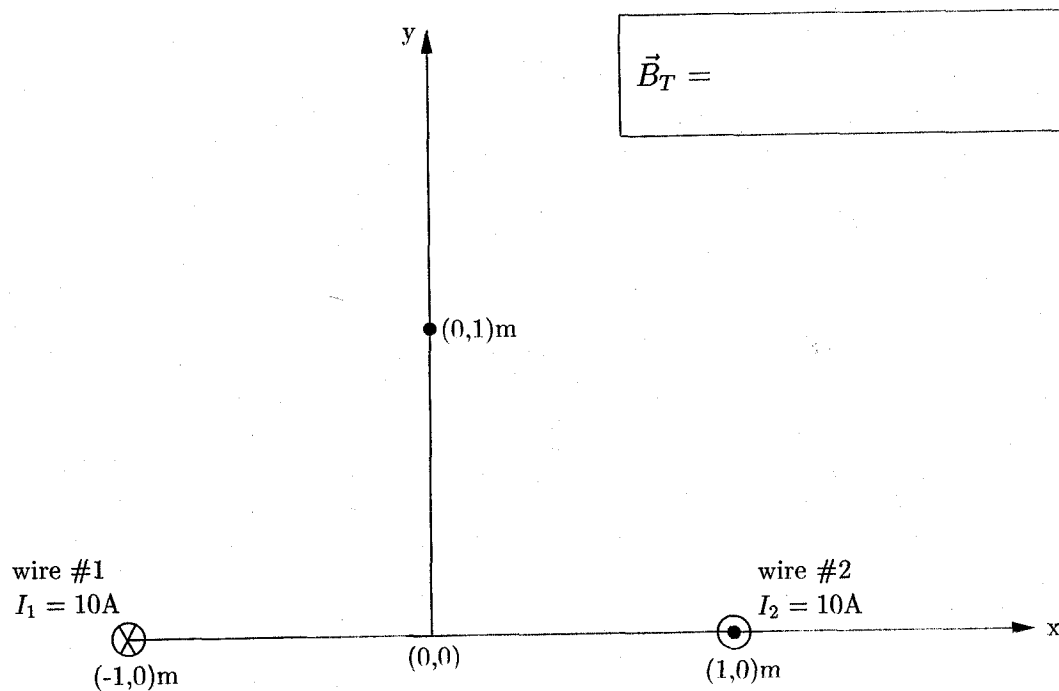


Figure 2

$\vec{B}_T =$

Question 3 (10 marks)

Page 4 of 11

The DC source in the circuit shown in Figure 3, supplies 600 watts. Determine  $R_1$  and  $R_2$ .

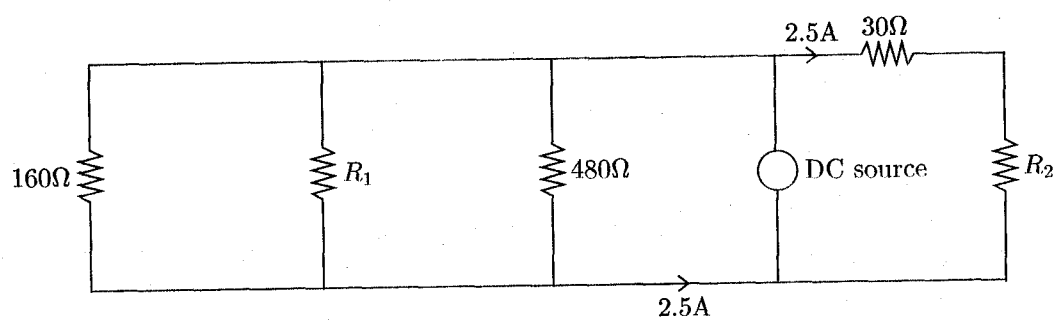


Figure 3

$$R_1 =$$

$$R_2 =$$

Question 4 (10 marks)

Page 5 of 11

For the circuit shown in Figure 4, is the 0.5A current source supplying or absorbing power and how much?

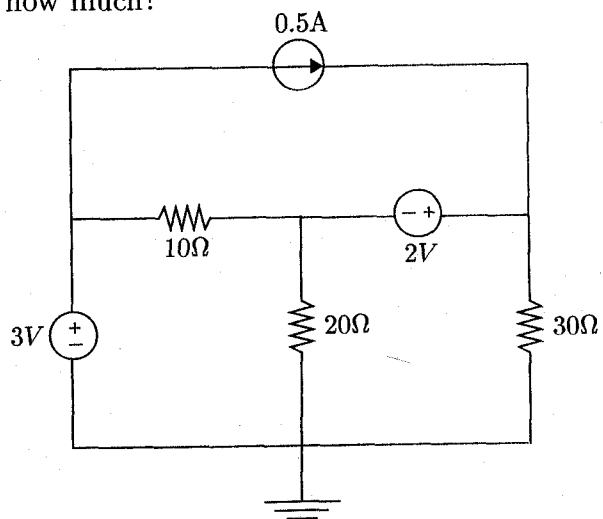


Figure 4

$P_{0.5A} =$

☐ Absorbed

☐ Supplied

Question 5 (10 marks)

Page 6 of 11

For the circuit shown in Figure 5, assume the operational amplifier is ideal and operating in the linear region. Determine the output voltage  $V_0$ .

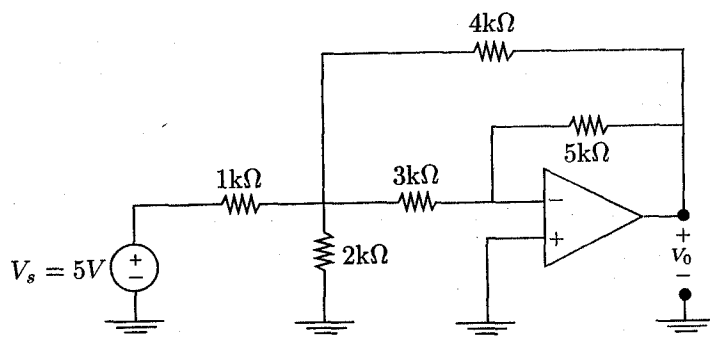


Figure 5

$V_0 =$

Question 6 (10 marks)

Page 7 of 11

A linear circuit is driven by an independent voltage source ( $V_s$ ) and an independent current source ( $I_s$ ). When the current source is turned off while the voltage source is set to  $10V$ , the output voltage is at  $3.5V$ . When the current source is set to  $1A$  while the voltage source remains at  $10V$ , the output voltage is now at  $0.5V$ . Express the output voltage in terms of the voltage source ( $V_s$ ) and the current source ( $I_s$ ).

$V_0 =$

Question 7 (10 marks)

Page 8 of 11

When a  $100\Omega$  resistor is connected across two-terminals of a linear circuit, the output voltage across the  $100\Omega$  resistor is at  $10V$ . When a  $200\Omega$  resistor is connected across the two-terminals, the output voltage is at  $12V$ . How much current would this linear circuit deliver to a  $250\Omega$  resistor?

$I =$



Question 8 (10 marks)

Page 9 of 11

The switch in the circuit shown in Figure 6 below has been opened for a long time. At  $t = 0$  the switch is closed. Determine:

- the current  $i_0(0^-)$  (3 marks)
- the current  $i_0(0^+)$  (3 marks)
- the current  $i_0(t)$  for  $t \geq 0$  (4 marks)

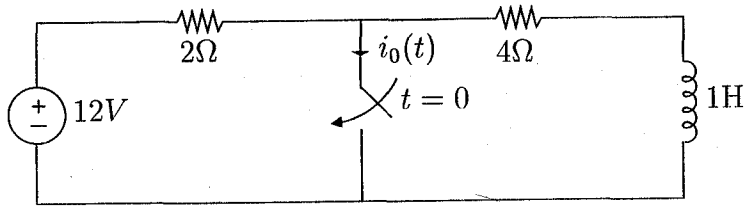


Figure 6

a)  $i_0(0^-) =$

b)  $i_0(0^+) =$

c)  $i_0(t) =$

The circuit in Figure 7 is in sinusoidal steady-state. Express the current through the capacitor as a function of time.

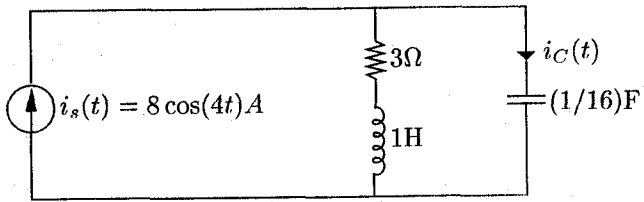


Figure 7

$$i_C(t) =$$

Question 10 (10 marks)

Page 11 of 11

An electrical load absorbs an average power of 8kw at a lagging power factor of 0.8. Find the complex power of the load.

S =