

Student name: \_\_\_\_\_

ID number: \_\_\_\_\_


*Solution*

University of Toronto  
Department of Electrical & Computer Engineering  
ECE110S – Electrical Fundamentals  
Quiz 3A – March 12, 2008, 4:30-5:00 PM

( $e = 1.6 \times 10^{-19}$  C,  $\epsilon_0 = 8.85 \times 10^{-12}$  F/m,  $\mu_0 = 4\pi \times 10^{-7}$  H/m,  $g = 9.81$  N/kg)

**Instructions:** Non-programmable calculators allowed. No other aids. Answer in the space provided on these sheets. The back sides of these sheets can be used as well. For full marks you must show methods, state UNITS and compute numerical answers when requested. **Please write in PEN, not pencil.**

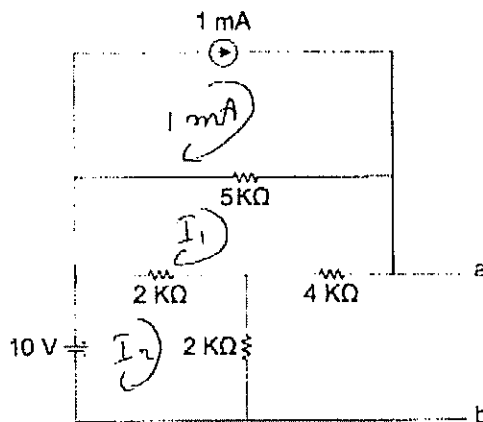1. (a) For the circuit below, use LOOP ANALYSIS to calculate  $v_{ab}$ , the voltage between the points  $a$  and  $b$ . (6 marks)
- (b) Calculate the load resistor  $R_L$  that must be connected between the two points  $a$  and  $b$  for maximum power transfer. (2 marks)
- (c) Express  $P_L$ , power absorbed by the load resistor, in terms of  $R_L$  and  $v_{ab}$ , and calculate the maximum  $P_L$ . (2 marks)





(a) KVL 1:  $5(I_1 - 1) + 4I_1 + 2(I_1 - I_2) = 0$   
 $11I_1 - 2I_2 = 5$

KVL 2:  $-10 + 2(I_2 - I_1) + 2I_2 = 0$   
 $-2I_1 + 4I_2 = 10$

$$\begin{cases} 11I_1 - 2I_2 = 5 \\ -2I_1 + 4I_2 = 10 \end{cases} \Rightarrow \begin{cases} I_1 = 1 \text{ mA} \\ I_2 = 3 \text{ mA} \end{cases}$$

$v_{ab} = 4I_1 + 2I_2 = 10 \text{ V}$

(b)  $R_L = R_{th} = (2 // 2 + 4) // 5$

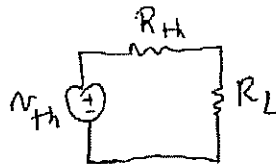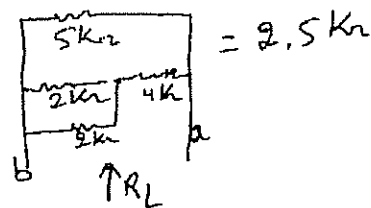

(c)  $P_L = \frac{v_{th}^2}{4R_{th}} = \frac{v_{ab}^2}{4R_L} = 10 \text{ mW}$


2. Consider the circuit shown below with an ideal op-amp.  $I_s$ ,  $V_s$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$  and  $R_5$  are known parameters.

- (a) Express  $v_i$  in terms of known parameters.  
 (b) Express  $v_{ab}$  in terms of known parameters.  
 (c) Express  $i_0$  in terms of known parameters.

(2 marks)

(3 marks)

(5 marks)

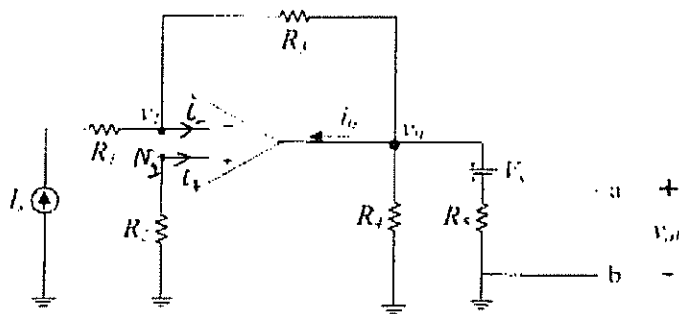

(a)  $i_+ = 0$  so  $v_+ = 0$  and  $v_- = v_+$  so  $v_- = 0$

(b) KCL:  $-I_s + i_- + \frac{v_- - v_0}{R_3} = 0 \Rightarrow v_0 = -R_3 I_s$

KVL:  $v_{ab} = v_0 - V_s = -I_s R_3 - V_s$

(c) KCL:  $i_0 + \frac{v_0 - v_-}{R_3} + \frac{v_0}{R_4} + \frac{v_0 - V_s}{R_5} = 0 \Rightarrow$

$$i_0 = -\frac{I_s R_3}{R_3} + I_s \frac{R_3}{R_4} + I_s \frac{R_3}{R_5} + \frac{V_s}{R_5}$$

$$= I_s \left( 1 + \frac{R_3}{R_4} + \frac{R_3}{R_5} \right) + \frac{V_s}{R_5}$$