



736A33AA-7E2C-4607-B871-771DA37540DA

term-test-2-8c488

#59 2 of 10

University of Toronto  
Faculty of Applied Science and Engineering  
**Department of Electrical and Computer Engineering**

ECE110S – Electrical Fundamentals  
Term Test 2 – March 24, 2022, 7:00 – 8:30 p.m.


( $e = 1.6 \times 10^{-19}$  C,  $\epsilon_0 = 8.85 \times 10^{-12}$  F/m,  $\mu_0 = 4\pi \times 10^{-7}$  H/m,  $g = 9.81$  N/kg)

ANSWER ALL QUESTIONS ON THESE SHEETS, USING THE BACK SIDE IF NECESSARY.

1. Non-programmable calculators (Casio FX-991MS & Sharp EL-520X) are allowed.
2. You are allowed a one page (8.5" x 11") double-sided aid sheet.
3. For full marks, you must show methods, state UNITS and compute numerical answers (when requested).
4. There is one extra blank page at the end for rough work.



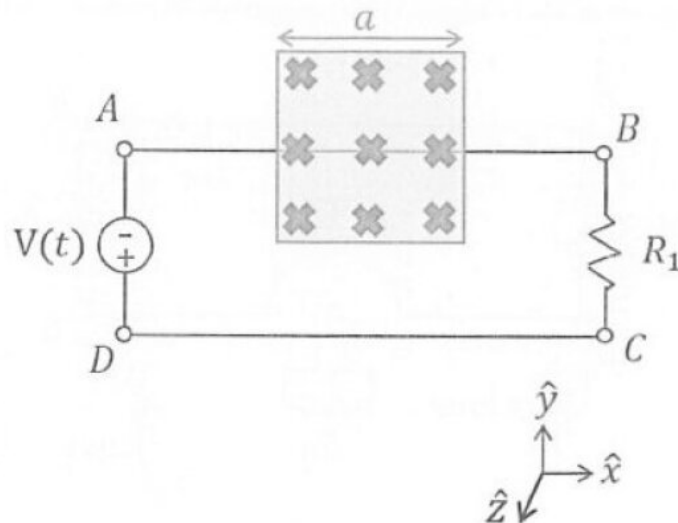Q1) Consider the following circuit (A-B-C-D) that consists of a voltage source  $V(t)$  and a resistor ( $R_1$ ). The segment of wire connecting nodes A and B overlaps with a uniform magnetic field ( $B = 2.5 \text{ mT}$ ) pointing into the x-y plane. The B field is confined within the square area, where  $a = 30 \text{ cm}$ .



- a) Determine the resistance ( $R_1$ ) needed for  $V(t) = 5 \text{ V}$  to exert a force of  $7.5 \text{ mN}$  on the segment of wire that overlaps with the magnetic field (B). [3 marks]

$$F = BIL$$

$$I = \frac{V}{R_1}$$

$$\therefore 7.5 \text{ mN} = (2.5 \text{ mT}) \left( \frac{5 \text{ V}}{R_1} \right) (30 \text{ cm})$$


$$R_1 = 0.5 \, \Omega$$

- b) What is the direction in which the wire is displaced by the magnetic field when  $V(t) = 2 \text{ V}$ ? [2 marks]

$$-\hat{y}, \text{ i.e., } \downarrow$$



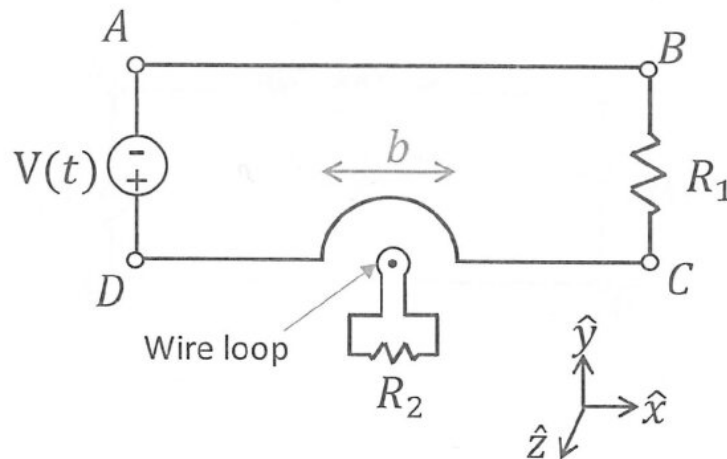Q1 cont.) The circuit is modified such that a segment of the wire between nodes C and D forms a semi-circle in the x-y plane, with a diameter of  $b = 40$  cm. There is a single wire loop (area =  $0.01 \text{ m}^2$ ) placed at the center of the semi-circle and connected to a second resistor ( $R_2$ ).



c) If  $V(t) = -5 \text{ V}$ , what is the direction of the magnetic field at the center of the loop wire? [2 marks]

$+\hat{z}$ , i.e.  $\odot$

d) If  $V(t)$  increases from  $0 \text{ V}$  to  $+5 \text{ V}$  over a period of  $1 \text{ s}$ , what is the direction of the electromotive force generated around the wire loop? [3 marks]


(i) clockwise direction

or

(ii) counter-clockwise direction



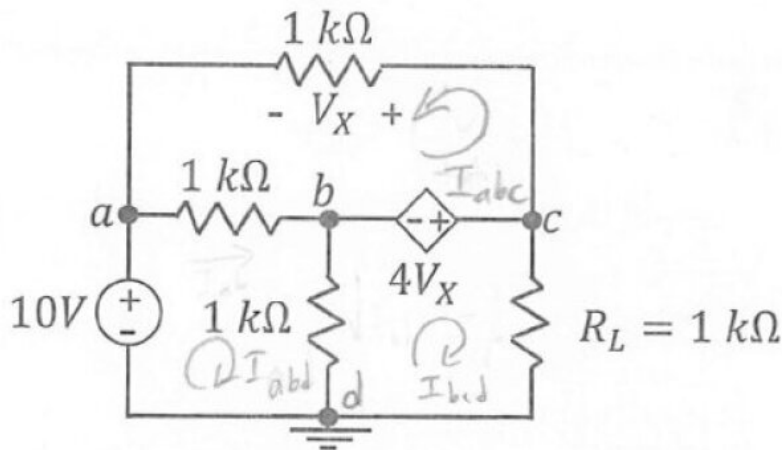Q2) For the circuit shown below,  $V_x$  is given in volts.



a) Compute  $V_x$ . [5 marks]

Mesh abd:

$$10 - (1k)(I_{abd} + I_{abc}) - (1k)(I_{abd} - I_{bcd}) = 0$$

$$2kI_{abd} + V_x - 1kI_{bcd} = 10$$

Mesh bcd:

$$4V_x - (1k)(I_{bcd}) - (1k)(I_{bcd} - I_{abd}) = 0$$

$$4V_x - 2kI_{bcd} + 1kI_{abd} = 0$$

Mesh abc:

$$4V_x - V_x - (1k)(I_{abc} + I_{abd}) = 0$$

$$2V_x - 1kI_{abd} = 0$$

Solving,

$$V_x = 5V$$

$$I_{abd} = 10mA$$

$$I_{bcd} = 15mA$$

N.B.  $I_{abc} = \frac{V_x}{1k}$

b) Compute the power in resistor  $R_L$ . Is it absorbed or supplied? [1 mark]

$$P = I^2 R = I_{bcd}^2 \cdot R_L$$

$$= (15mA)^2 \cdot (1k\Omega)$$

$$P_L = 225mW$$

absorbed

since resistors  
do not supply power



- c) Compute the power in the independent voltage source. Is it absorbed or supplied? [2 marks]

$$P = IV = I_{abd} \cdot 10V$$
$$= (10 \text{ mA})(10 \text{ V})$$

$$P = 100 \text{ mW}$$

Supplied, since current runs through it from the -ve to +ve terminals

- d) Compute the power in the dependent voltage source. Is it absorbed or supplied? [2 marks]

$$P = IV = (I_{abc} + I_{bcd})(4V_x)$$
$$= \left(\frac{5V}{1k\Omega} + 15 \text{ mA}\right)(4.5 \text{ V})$$


$$P = 400 \text{ mW}$$

Supplied for similar reasons as (c)



Q3) Solve the following circuits:

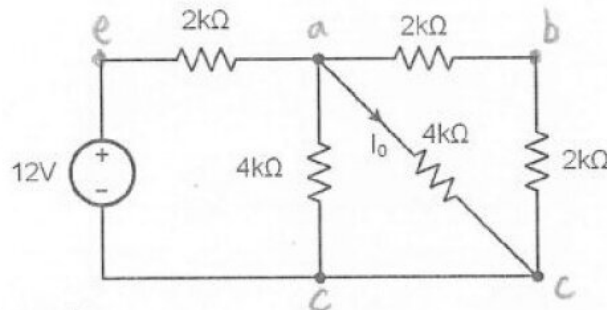- a) Find  $I_0$  in the network below using the homogeneity (scaling) property of linear systems.  
[5 marks]




Let  $I'_0 = 1 \text{ mA}$ , and the voltage of the independent source be  $V_0$ .

By homogeneity,  $\frac{12 \text{ V}}{V_0} = \frac{I_0}{I'_0} \Rightarrow I_0 = \frac{12 \times 10^{-3}}{V_0}$

$$V_{ac} = I'_0 \cdot (4 \text{ k}\Omega)$$

$$= 4 \text{ V}$$

Combine resistors:

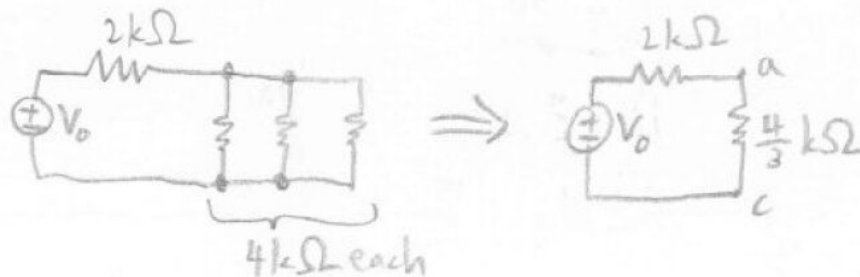

Voltage divider:

$$V_{ac} = \frac{\frac{4}{3} \text{ k}}{\frac{4}{3} \text{ k} + 2 \text{ k}} V_0$$


$$V_0 = 10 \text{ V}$$

$$I_0 = \frac{12 \times 10^{-3}}{10}$$


$$\therefore \boxed{I_0 = 1.2 \text{ mA}}$$




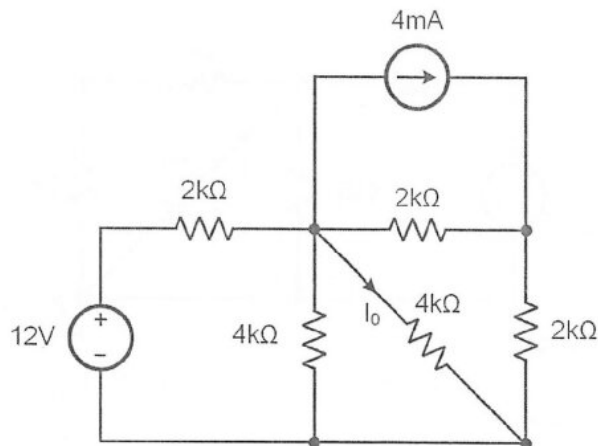
(b) Find  $I_0$  in the network below using the superposition (additivity) property of linear systems. [5 marks]



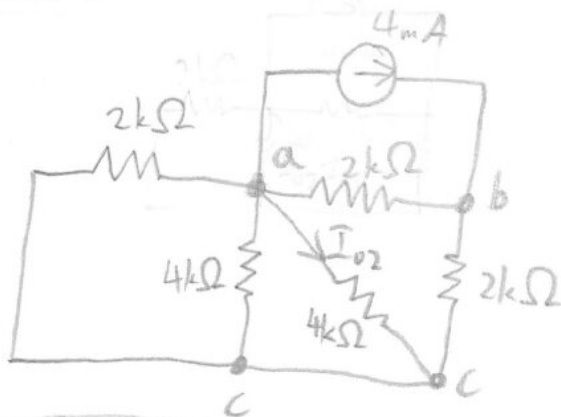Set the current source to zero, it becomes an open circuit.  
This is what we did in part (a),  $\therefore I_{01} = 1.2 \text{ mA}$   
Set the voltage source to zero, it becomes a short circuit.



Source transformation;

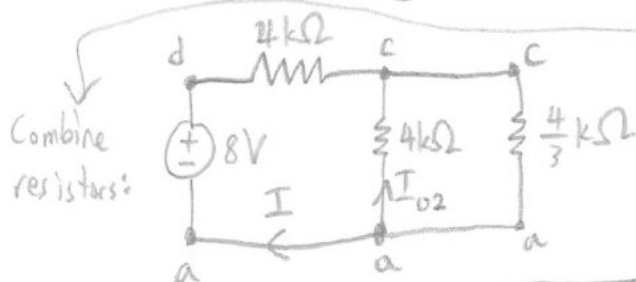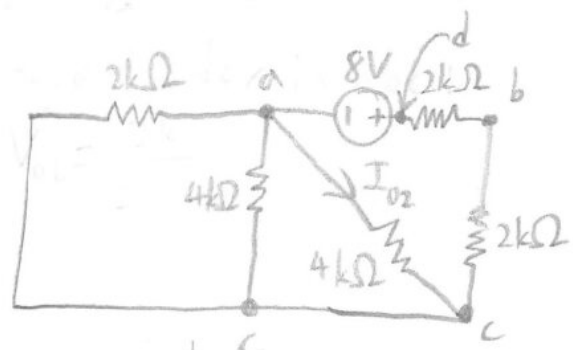

$$\therefore I = \frac{8V}{5k\Omega} = 1.6 \text{ mA}$$

Current division:

$$-I_{02} = \frac{\frac{4}{3}k}{\frac{4}{3}k + 4k} I$$

(cont'd on next page)



For Extra work

(cont'd from Q3(b))

$$\boxed{I_{o2} = -0.4 \text{ mA}}$$

By the additive property of linear systems,

$$I_o = I_{o1} + I_{o2} = 1.2 \text{ mA} - 0.4 \text{ mA}$$

$$\boxed{I_o = 0.8 \text{ mA}}$$






0A1B1138-CDB6-46C7-9D34-03A1C2436B6C


term-test-2-8c488

#59 10 of 10

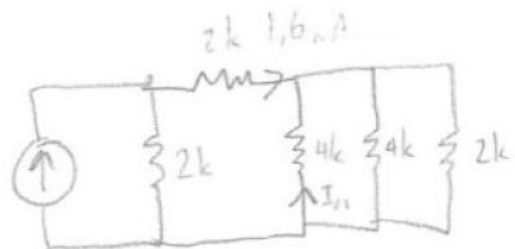

$$V_{TH} =$$

$$I_{TH} = \frac{V_{TH}}{R_{TH}}$$

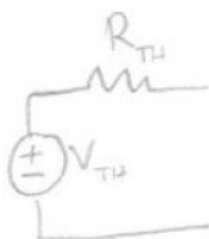

$$I_o = \frac{3V}{6k} = 0.5mA \quad I_o' = 1mA$$
$$= \frac{3V}{V_o} \cdot I_o' \quad V_o = 6k \cdot 1mA = 6V$$