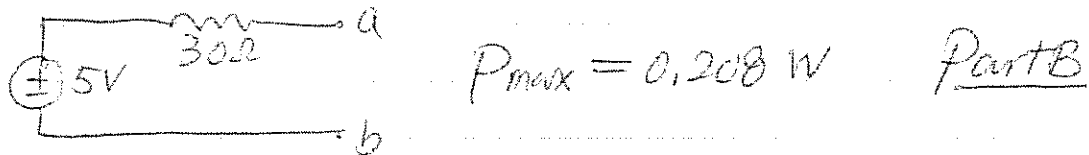


Final 2006 Answer Key

Q1. Part A $q_3 = +0.68 \text{ nC}$ Part B $v = \frac{Q}{4\pi\epsilon_0 r^2 B}$


Q2. $V_0 = 2 \text{ V}$, $P_{0.5 \text{ A}} = 6 \text{ W}$ Part A



Q3. Part A $I_1 = -8 \text{ mA}$ Part B $V_0 = +2.4 \text{ V}$
 $I_2 = 36 \text{ mA}$

Q4. $i_L(0^-) = -5 \text{ A}$ $\tau = 200 \mu\text{s}$
 $i_L(0^+) = -5 \text{ A}$ $i_L(t) = -2 - 3e^{-5000t} \text{ A}$
 $v_x(0^-) = 0 \text{ V}$ $v_L(t) = 60e^{-5000t} \text{ V}$
 $v_L(0^+) = 60 \text{ V}$
 $i_L(\infty) = -2 \text{ A}$

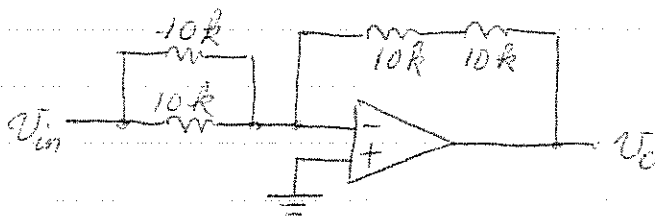Q5. Part A $R_{\text{in}} = 5 \text{ k}\Omega$ Part B $dv/dt = -2 \text{ A/A}$
 $V_0 = -10 \text{ V}$



Q6. $I = 200 \angle -37^\circ \text{ A}_{\text{RMS}}$
 $Z_{\text{LINE}} = 0.05 + j0.075 \Omega$
 $V_g = 257 \angle 1.34^\circ \text{ V}_{\text{RMS}}$