

ECE110 - Quiz #5

Only non-programmable calculators are allowed.

Duration: 30 Minutes

First Name: _____ Last Name: _____

Student #: _____ Tutorial Section: _____

[5 Marks] Determine Thevenin's equivalent of the following circuit.

