

UNIVERSITY OF TORONTO
FACULTY OF APPLIED SCIENCE AND ENGINEERING
FINAL EXAMINATION, APRIL 2008

First Year – Computer, Electrical, Industrial, Mechanical, Materials, and
TRACK ONE (General) Engineering Programs.

ECE 110H1 S – ELECTRICAL FUNDAMENTALS

Exam. Type: A

Examiners – B.L. Bardakjian, L. de Windt, P. Herman, L. Qian,
C. Sarris, and B. Wang

NAME : (PLEASE PRINT)	<div style="border-bottom: 1px solid black; height: 1.2em; margin-bottom: 5px;"></div> FAMILY NAME	<div style="border-bottom: 1px solid black; height: 1.2em; margin-bottom: 5px;"></div> GIVEN NAME
STUDENT NUMBER :		

EXAMINATION TYPE : Type A – Paper for which no data are permitted other than the information printed on the examination paper.

CALCULATORS : ONLY Non-programmable scientific type allowed (models as specified in the Faculty Calendar).

DURATION : 2.5 hours

- INSTRUCTIONS :
- DO NOT UNSTAPLE THIS EXAM. BOOK.
 - Answer all six questions.
 - All six questions are of equal weight.
 - All work is to be done on these pages. Show methods, compute numerical results when requested and state units.
 - Place your final answer in the corresponding box. You may use the back of the preceding page for rough work.

$e = 1.6 \times 10^{-19} \text{C}, \quad \epsilon_o = 8.85 \times 10^{-12} \text{ F/m}, \quad \mu_o = 4\pi \times 10^{-7} \text{ H/m}$
--

Question	Mark
1	
2	
3	
4	
5	
6	
Total	

Question 1 - Electricity and Magnetism

Part A

The device shown in Fig. 1A is called a velocity selector and its operation is as follows: Charges q launched into the chamber from its left aperture with velocity $\vec{v} = v \hat{i}$, should be able to exit the chamber from its right aperture, moving along a linear trajectory, only if $v = v_0$.

If the electric field in the chamber is $\vec{E} = -E_0 \hat{j}$, determine the magnetic field (magnitude in terms of E_0 , v_0 , q and direction) needed for the device to operate as described above. [4 marks]

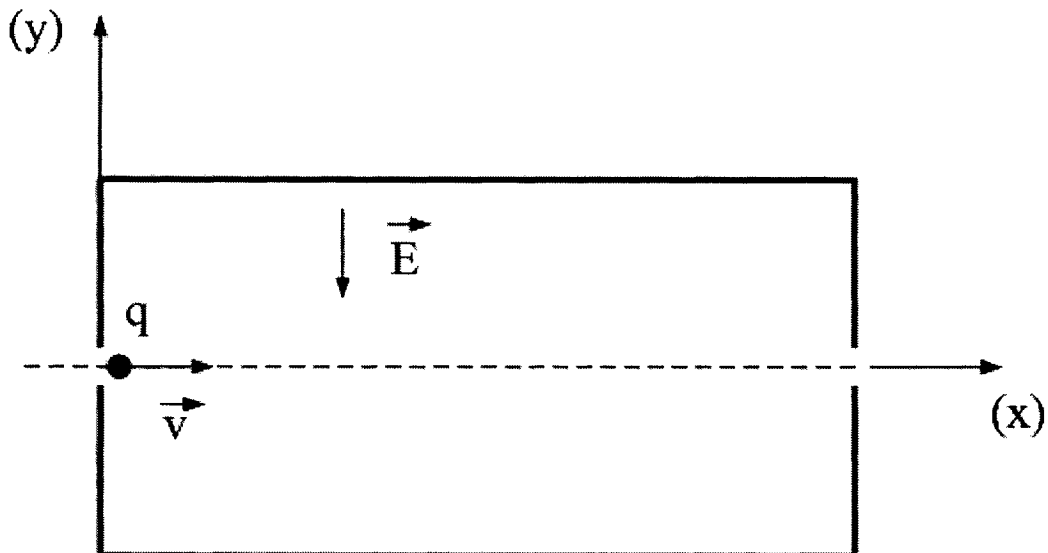


Figure 1A: Velocity selector

$\vec{B} =$

Question 1 - Electricity and MagnetismPart B

A small conducting loop of area $S=2 \text{ cm}^2$ moves near an infinite line current I , and includes a resistor $R=5 \Omega$, as shown in Fig. 1B.

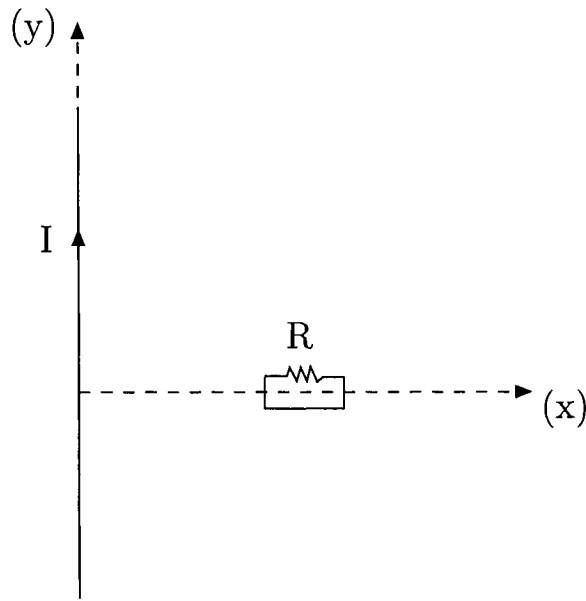


Figure 1B: Small loop and infinite line current.

- i) Determine whether there is an induced current in the loop and show the direction of that current, if the loop moves with a constant velocity in the:
 - $+x$ direction;
 - $+y$ direction. [2 marks]
- ii) Assume that the magnetic field produced by the wire is almost constant throughout the loop area and equal to its value at the center of the loop. Find the current I of the vertical wire if the loop current is $I_{loop}=1 \mu\text{A}$ at $(x=0.25 \text{ m}, y=0)$, when the loop moves with a constant velocity $\vec{v}=10 \text{ m/sec } \hat{i}$. [4 marks]

You may need: $\frac{d}{dt} \left(\frac{1}{x} \right) = -\frac{1}{x^2} \frac{dx}{dt}$.

$I =$

Question 2 – DC Circuits

Consider the circuit shown in Fig. 2.1.

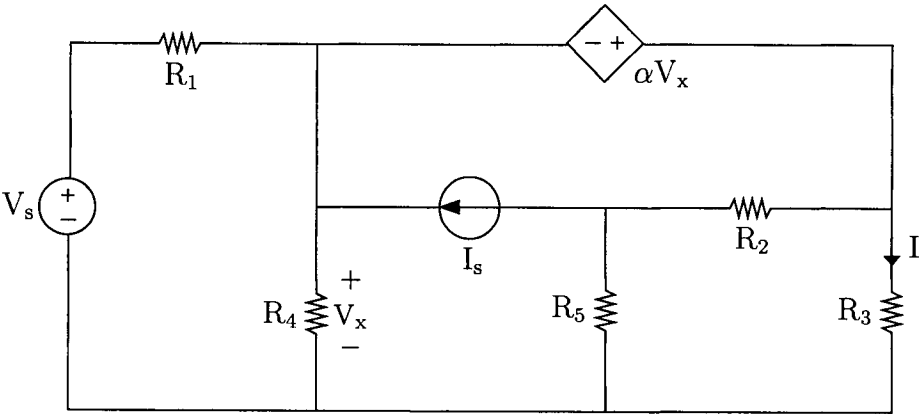


Fig. 2.1

$V_s = 3V, I_s = 10mA, \alpha = 2,$
 $R_1 = 4k\Omega, R_2 = 3k\Omega, R_3 = 1k\Omega, R_4 = 2k\Omega, R_5 = 6k\Omega$

- (a) Use LOOP or NODAL analysis to find I. [7 marks]
- (b) If the values of V_s and I_s are doubled
(i.e., V_s is replaced by $V'_s = 6V$ and I_s
is replaced by $I'_s = 20mA$), find the
new current I' passing through R_3 . [3 marks]

$I =$
$I' =$

Question 3**Part A**

Consider the case of maximum power that can be transferred to the load R_L in the circuit shown in Figure 3A. Determine:

- i) The load R_L . [2 marks]
- ii) The maximum power. [3 marks]

i) $R_L =$

ii) $P_{\max} =$

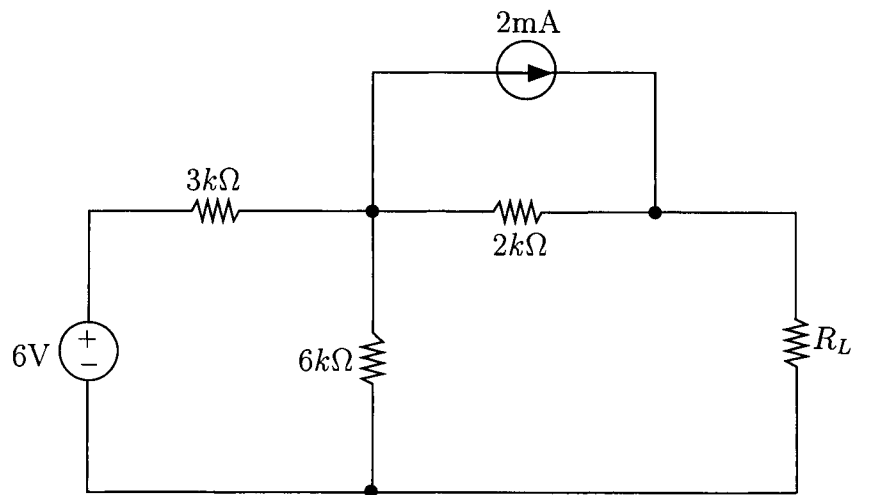


Figure 3A

Question 3**Part B**

Consider the circuit shown in Figure 3B. Determine:

- i) The Thévenin equivalent source. [1 mark]
- ii) The Thévenin equivalent resistance. [3 marks]
- iii) The Norton equivalent source. [1 mark]

i) $V_{th} =$

ii) $R_{th} =$

iii) $I_N =$

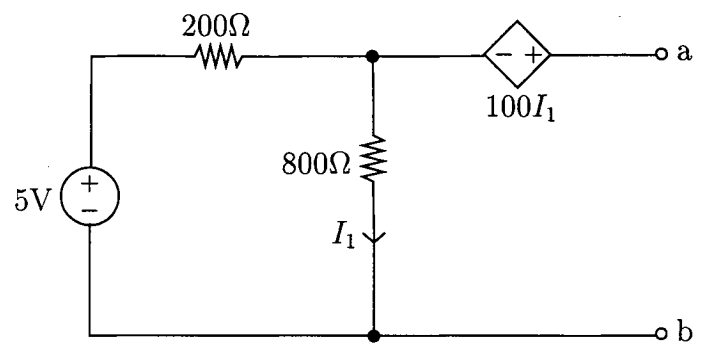


Figure 3B

Question 4

For the circuit shown in Figure 4, the operational amplifiers are ideal and operating in their linear region. Determine in terms of v_i :

- i) The voltage v_a [2 marks]
- ii) The voltage v_b [2 marks]
- iii) The voltage v_0 [2 marks]
- iv) The current i_a [2 marks]
- v) The current i_b [2 marks]

- i) $v_a =$
- ii) $v_b =$
- iii) $v_0 =$
- iv) $i_a =$
- v) $i_b =$

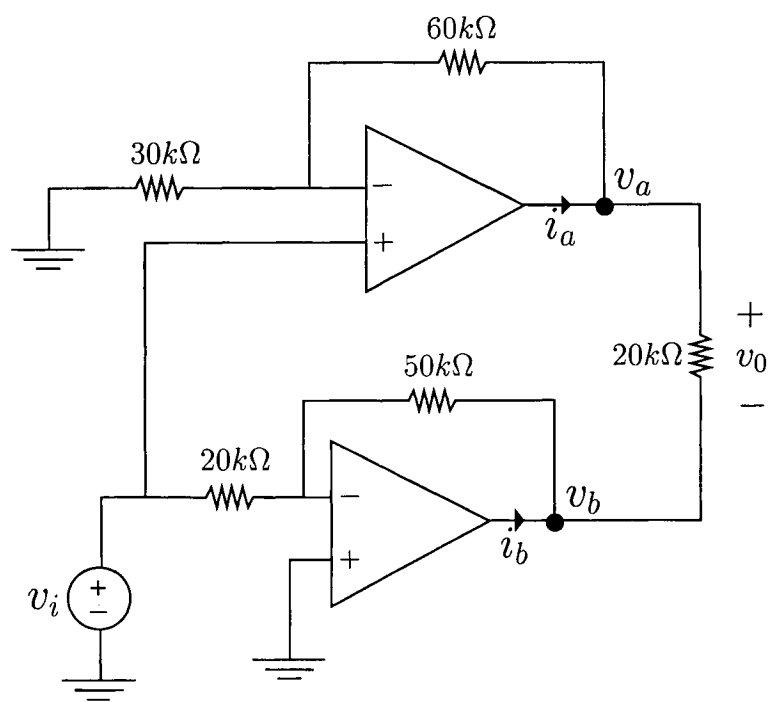


Figure 4

Question 5

For the circuit shown in Figure 5, the switch has been closed for a long time and it opens at $t = 0$.

- i) Find the voltage, $V_C(0^-)$ and the current, $i_L(0^-)$; [2 marks]
- ii) Find the voltage, $V_1(0^+)$ and the current, $i_L(0^+)$; [2 marks]
- iii) Find the voltage, $V_1(\infty)$ and the current, $i_L(\infty)$; [2 marks]
- iv) Find the time constants associated with the capacitor, τ_C and that of the inductor, τ_L ; [2 marks]
- v) Sketch the transient responses, $V_1(t)$ and $i_L(t)$ for $t > 0$. [2 marks]

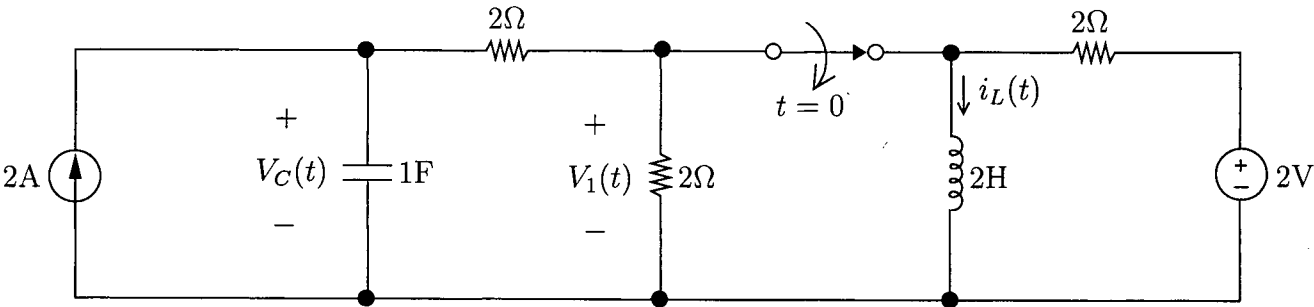


Figure 5

$V_C(0^-) =$	$i_L(0^-) =$
$V_1(0^+) =$	$i_L(0^+) =$
$V_1(\infty) =$	$i_L(\infty) =$
$\tau_C =$	$\tau_L =$

Question 6 – AC Circuit

The circuit below is in a sinusoidal steady state operating at a frequency of 400 Hz.

- i) State the values of the capacitor and inductor. [2 marks]
- ii) Find the phasor voltage V_{ab} [4 marks]
- iii) Determine the average power absorbed by the circuit. [4 marks]

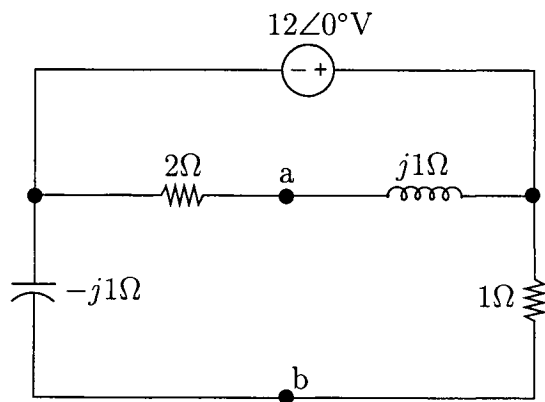


Figure 6

- i) $C =$
 $L =$
- ii) $V_{ab} =$
- iii) $P_A =$