

Final 2007 Answer Key

Q1. Part A $\bar{E} = 4 \times 10^{13} \text{ G} \cdot \text{J} [\text{N/C}]$

Coordinates: $(1.5 \text{ cm}, 0)$

Part B i) 4)

ii) 0.141 A (cw)

Q2. Part A $V_1 = -4 \text{ V}$


$V_2 = 1 \text{ V}$

$I_1 = 0.5 \text{ A}$

$I_2 = -0.1 \text{ A}$

Part B $i = -\frac{1}{3} \text{ A}$

Q3. Part A $P_{\max} = 18 \text{ W}$

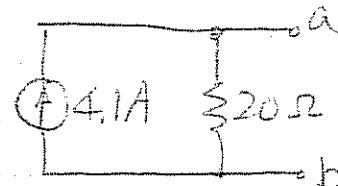

Q4. i) $q_1(t=0) = 3 \times 10^{-4} \text{ C}$

$q_2(t=0) = 3 \times 10^{-4} \text{ C}$

$q_3(t=0) = 2 \times 10^{-4} \text{ C}$

ii) $W_e(t=0) = 2.5 \times 10^{-3} \text{ J}$

iii) $C_{eq} = 50 \mu\text{F}$

iv) $10^{-3} \frac{dV_c(t)}{dt} + V_c(t) = 0$

v) $\tau = 1 \text{ ms}$

vi) $V_c(t) = 10 e^{-10^3 t}$

vii) $i(t=0^+) = 0.5 \text{ A}$

viii) $t_x = 6.9 \times 10^4 \text{ s}$

Q5. i) $R_{in} = \infty$

ii) $V_{D1} = 0.2 \text{ V}$

Q6. $i(t) = 10.5 \cos(377t + 20^\circ) \text{ A}$

iii) $V_{D2} = 0.4 \text{ V}$

iv) $V_{D3} = -1.6 \text{ V}$

$Q_{load} = -340.4 \text{ VAR}$

v) $V_{D4} = 2.4 \text{ V}$

vi) $i_F = 0.03 \text{ mA}$

$Z_{load} = 10 \angle -20^\circ \text{ ohms}$

vii) $i_o = 0.05 \text{ mA}$

$R = 9.4 \Omega, C = 780 \mu\text{F}$